



國立勤益科技大學


National Chin-Yi University of Technology

Introduction to VLSI Circuits and Systems

積體電路概論

Chapter 12

Arithmetic Circuits in CMOS VLSI

 

賴秉樑

Dept. of Electronic Engineering

National Chin-Yi University of Technology

Fall 2007

Outline

- ❑ Bit Adder Circuits
- ❑ Ripple-Carry Adders
- ❑ Carry Look-Ahead Adders
- ❑ Other High-Speed Adders
- ❑ Multipliers

Half-Adder Circuits

- Consider two binary digit x and y , and the binary sum is denoted by $x + y$ such that

$$\begin{aligned} 0 + 0 &= 0 \\ 0 + 1 &= 1 \\ 1 + 0 &= 1 \\ 1 + 1 &= 10 \end{aligned} \quad (12.1)$$

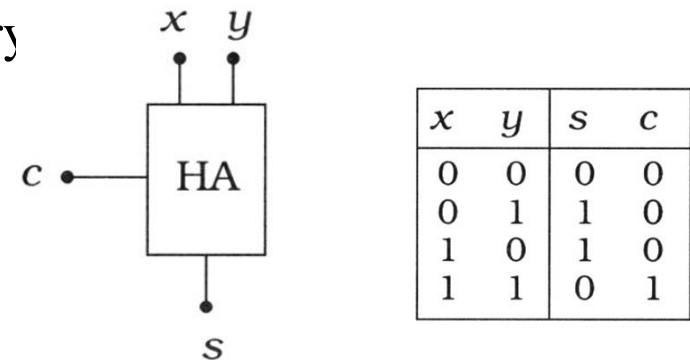


Figure 12.1 Half-adder symbol and operation

- A half-adder has 2 inputs (x and y) and 2 outputs (the sum s and the carry-out c)

$$\begin{aligned} s &= x \oplus y \\ c &= x \cdot y \end{aligned} \quad (12.2)$$

 


Figure 12.2 Half-adder logic diagram

Full-Adder Circuits

- Adding n -bit binary words

$$\begin{array}{r} a_3 a_2 a_1 a_0 \\ + b_3 b_2 b_1 b_0 \\ \hline c_4 \ s_3 s_2 s_1 s_0 \end{array} \quad (12.3)$$

- In the standard carry algorithm, each of the i -th columns ($i = 0, 1, 2, 3$) operates according to the full-adder equation

$$\begin{array}{r} c_i \\ a_i \\ + b_i \\ \hline c_{i+1} \ s_i \end{array} \quad (12.4)$$


- Expressions for the network are

$$s_i = a_i \oplus b_i \oplus c_i \quad (12.5)$$

$$c_{i+1} = a_i \cdot b_i + c_i \cdot (a_i \oplus b_i)$$

or

 
$$c_{i+1} = a_i b_i + c_i \cdot (a_i + b_i) \quad (12.6)$$



(a) NAND2 logic

(b) NOR-based network

Figure 12.3 Alternate half-adder logic networks

 

a_i	b_i	c_i	s_i	c_{i+1}
0	0	0	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1
0	0	1	1	0
0	1	1	0	1
1	0	1	0	1
1	1	1	1	1

Figure 12.4 Full-adder symbol and function table

Complementary Pass-transistor Logic

□ Dual-rail complementary pass-transistor logic (CPL)

$$a_i \oplus b_i \text{ and } \overline{a_i \oplus b_i} \quad (12.7)$$


$$s_n = \overline{(a_i \oplus b_i)} \cdot c_i + (a_i \oplus b_i) \cdot \overline{c_i} \quad (12.8)$$

$$\overline{a_i} \cdot b_i + \overline{b_i} \cdot \overline{c_i} \quad (12.9)$$


$$\overline{b_i} \cdot c_i + a_i \cdot b_i \quad (12.10)$$

$$\overline{a_i} \cdot \overline{b_i} + b_i \cdot \overline{c_i} \quad (12.11)$$

 
$$b_i \cdot c_i + a_i \cdot \overline{b_i} \quad (12.12)$$



(a) 2-input array

 


(b) Sum circuit

 


(c) Carry circuit

Figure 12.5 CPL full-adder design


Full-Adder Circuits (1/2)

 

(a) Gate-level logic

 

(b) HA-based design

 

(a) Standard nFET logic

Figure 12.6 Full-adder logic networks


 


Figure 12.7 AOI full-adder logic

 

(b) Mirror circuit

Figure 12.8 Evolution of carry-out circuit

Full-Adder Circuits (2/2)

 


Figure 12.9 Mirror AOI CMOS full-adder

 


Figure 12.10 Transmission-gate full-adder circuit

Outline

- ❑ Bit Adder Circuits
- ❑ Ripple-Carry Adders
- ❑ Carry Look-Ahead Adders
- ❑ Other High-Speed Adders
- ❑ Multipliers

Ripple-Carry Adders

 


Figure 12.11 An n-bit adder

 


Figure 12.13 Worst-case delay through the 4-bit ripple adder

 


Figure 12.12 A 4-bit ripple-carry adder

 


Figure 12.14 4-bit adder-subtractor circuit

Outline

- ❑ Bit Adder Circuits
- ❑ Ripple-Carry Adders
- ❑ Carry Look-Ahead Adders
- ❑ Other High-Speed Adders
- ❑ Multipliers

Carry Look-Ahead Adders (1/3)

 


Figure 12.15 Basis of the carry look-ahead algorithm

 


Figure 12.16 Logic network for 4-bit CLA carry bits



 


Figure 12.17 Sum calculation using the CLA network


Carry Look-Ahead Adders (2/3)

 


(a) C_1 logic

 

(b) C_2 logic

 


(c) C_3 logic

 


(d) C_4 logic


Figure 12.18 nFET logic arrays for the CLA terms

 

(a) Complementary

 


(b) Pseudo nMOS

 


(c) Dynamic

Figure 12.19 Possible uses of the nFET logic arrays in Figure 12.18

Carry Look-Ahead Adders (3/3)

 

(a) Series-parallel circuit

 

(b) Mirror equivalent

Figure 12.20 Static CLA mirror circuit

 


Figure 12.21 Static mirror circuit for C_2

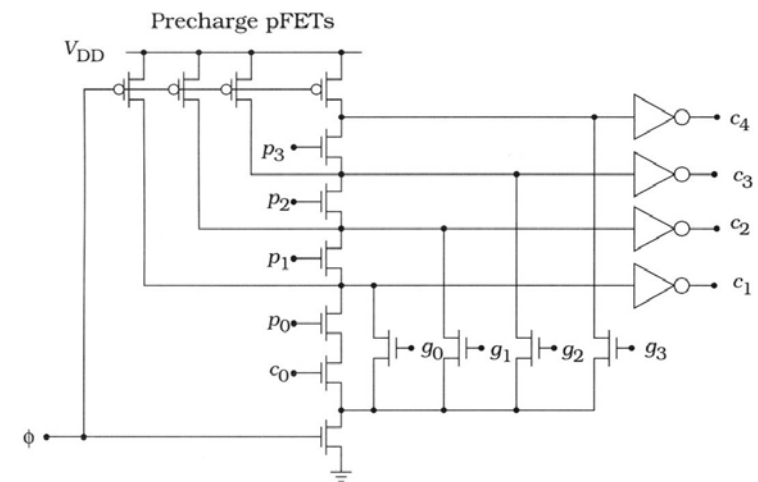


Figure 12.22 MODL carry circuit

Manchester Carry Chains

a_i	b_i	p_i	g_i	k_i
0	0	0	0	1
0	1	1	0	0
1	0	1	0	0
1	1	0	1	0

Figure 12.23 Propagate, generate, and carry-kill values



 


Figure 12.24 Switching network for the carry-out equation

 

(a) Static circuit

 

(b) Dynamic circuit

Figure 12.25 Manchester circuit styles

 


Figure 12.26 Dynamic Manchester carry chain

Extension to Wide Adders (1/2)

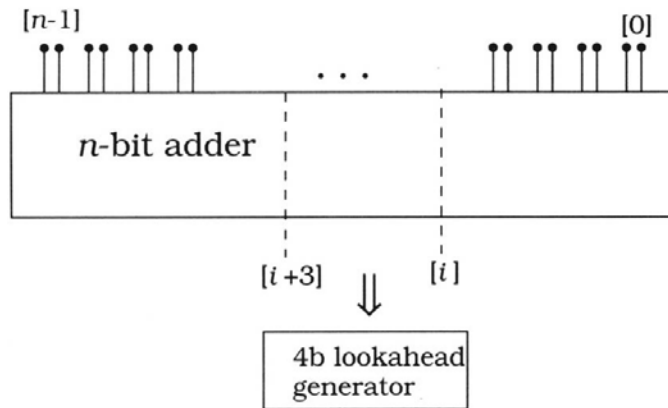


Figure 12.27 An n-bit adder network

 


Figure 12.28 4-bit lookahead carry generator signals

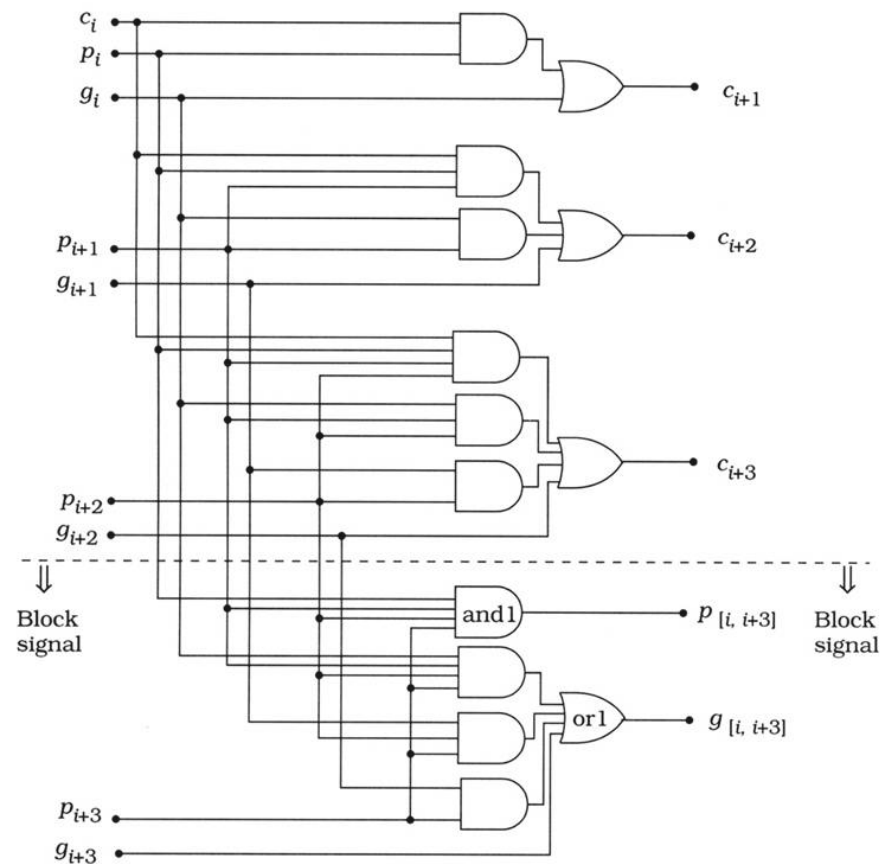


Figure 12.29 Block lookahead generator logic

Extension to Wide Adders (2/2)

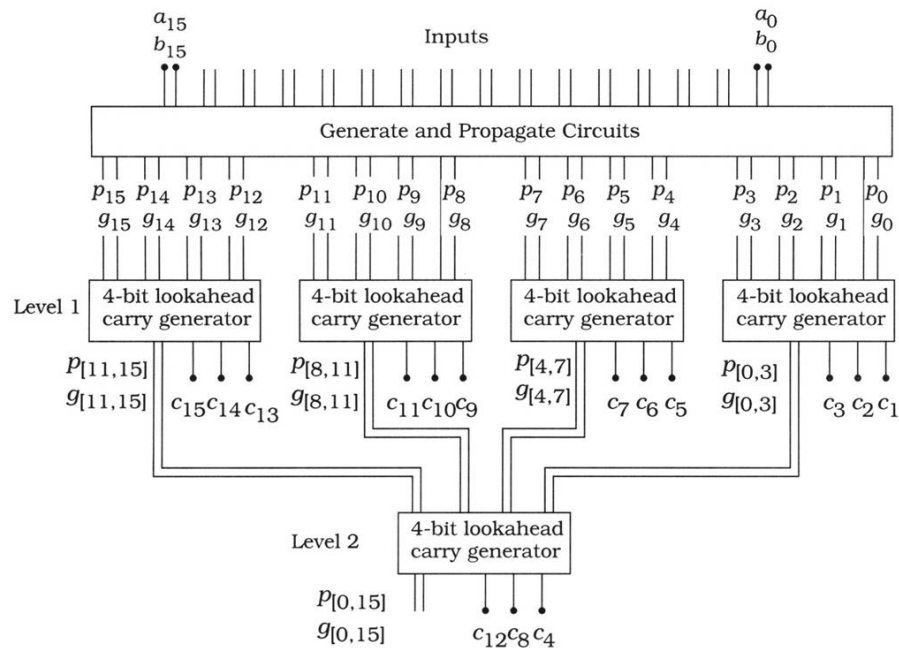


Figure 12.30 Multilevel CLA block scheme for a 16-bit adder


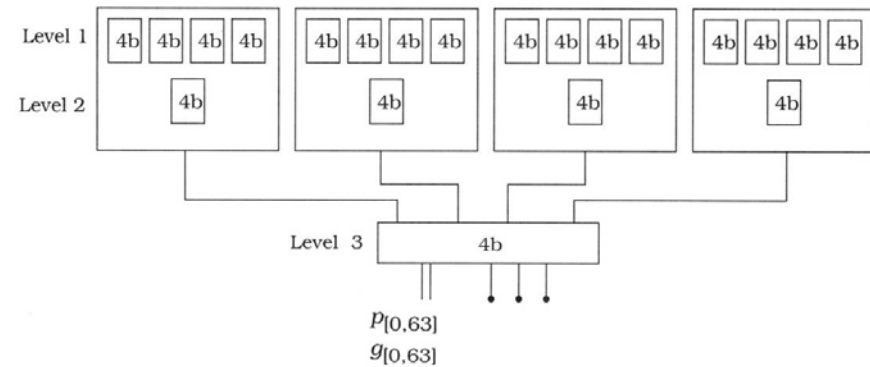


Figure 12.31 64-bit CLA architecture

Outline

- ❑ Bit Adder Circuits
- ❑ Ripple-Carry Adders
- ❑ Carry Look-Ahead Adders
- ❑ Other High-Speed Adders
- ❑ Multipliers

Carry-Skip Circuits

 

(a) Carry-skip logic


 


Figure 12.33 A 16-bit adder using carry-skip circuits

 

(b) Generalization

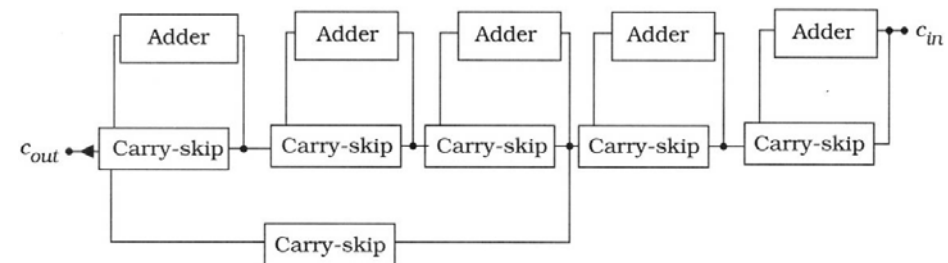


Figure 12.34 A 2-level carry-skip adder

Figure 12.32 Carry-skip circuitry

Carry-Select Adders



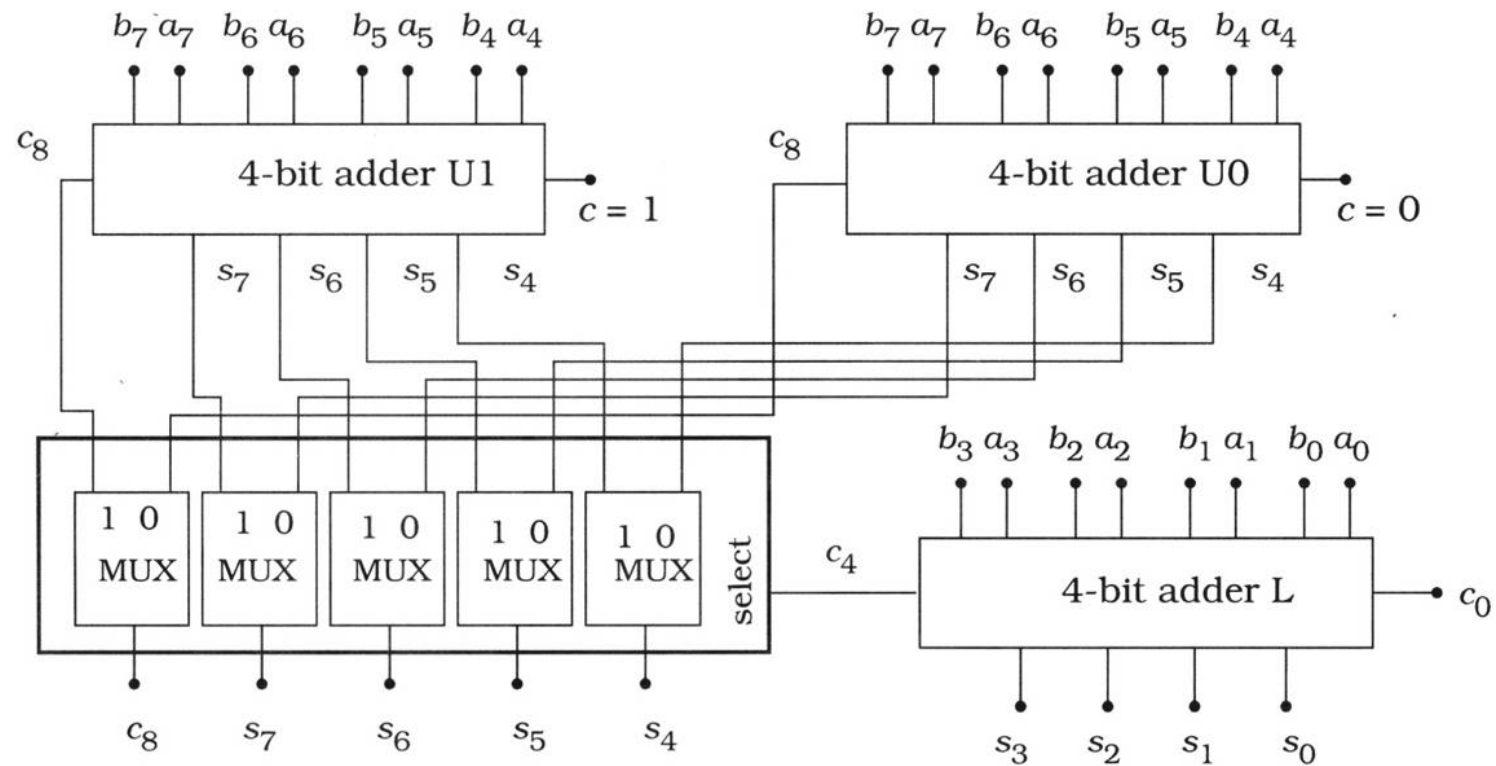


Figure 12.35 8-bit carry-select adder

Carry-Save Adders

 

(a) Symbol

 

(b) 3-to-2 reduction

Figure 12.36 Basic of a carry-save adder

 
 


Figure 12.37 Creation of an n -bit carry-save adder

Outline

- ❑ Bit Adder Circuits
- ❑ Ripple-Carry Adders
- ❑ Carry Look-Ahead Adders
- ❑ Other High-Speed Adders
- ❑ Multipliers

Multipliers (1/2)

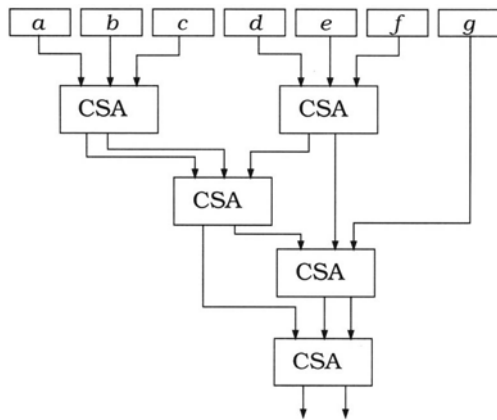


Figure 12.38 A 7-to-2 reduction using carry-save adders

 


Figure 12.39 Bit-level multiplier

 


Figure 12.40 Multiplication of two 4-bit words

 


Figure 12.41 Shift register for multiplication or division by a factor of 2

Multipliers (2/2)

$$\begin{array}{r}
 \begin{array}{cccc}
 & a_3 & a_2 & a_1 & a_0 \\
 \times & b_3 & b_2 & b_1 & b_0 \\
 \hline
 & (a_3 & a_2 & a_1 & a_0) \times b_0 & (a \times b_0) 2^0 \\
 & (a_3 & a_2 & a_1 & a_0) \times b_1 & (a \times b_1) 2^1 \\
 & (a_3 & a_2 & a_1 & a_0) \times b_2 & (a \times b_2) 2^2 \\
 + & (a_3 & a_2 & a_1 & a_0) \times b_3 & (a \times b_3) 2^3 \\
 \hline
 p_7 & p_6 & p_5 & p_4 & p_3 & p_2 & p_1 & p_0 & \text{product}
 \end{array}
 \end{array}$$

Figure 12.42 Alternate view of multiplication process

 


Figure 12.43 Using a product register for multiplication

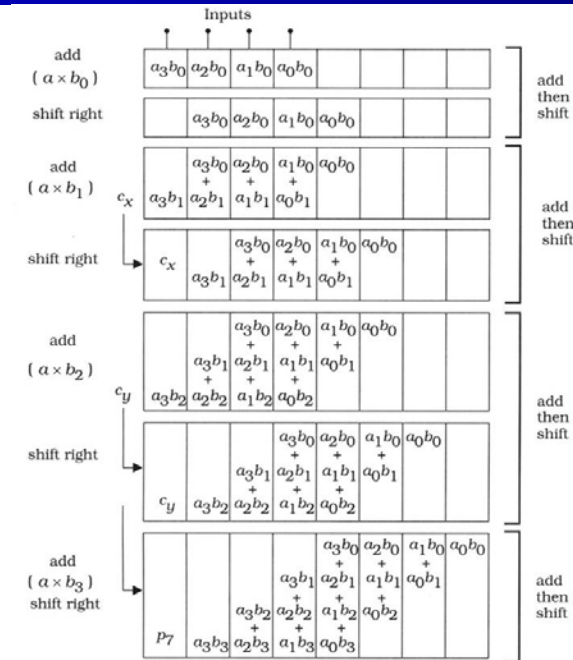


Figure 12.44 Shift-right multiplication sequence

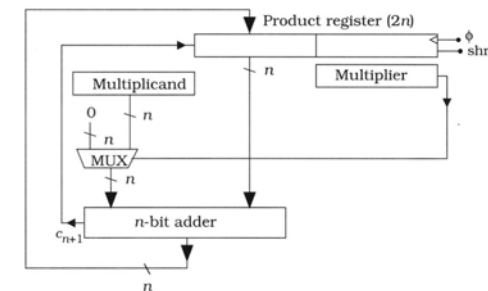


Figure 12.45 Register-based multiplier network

Array Multipliers

 


Figure 12.46 An array multiplier

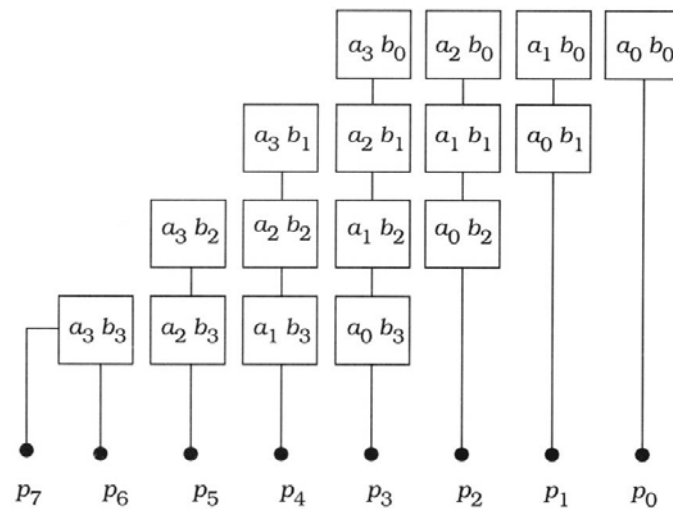


Figure 12.47 Modularized view of the multiplication sequence

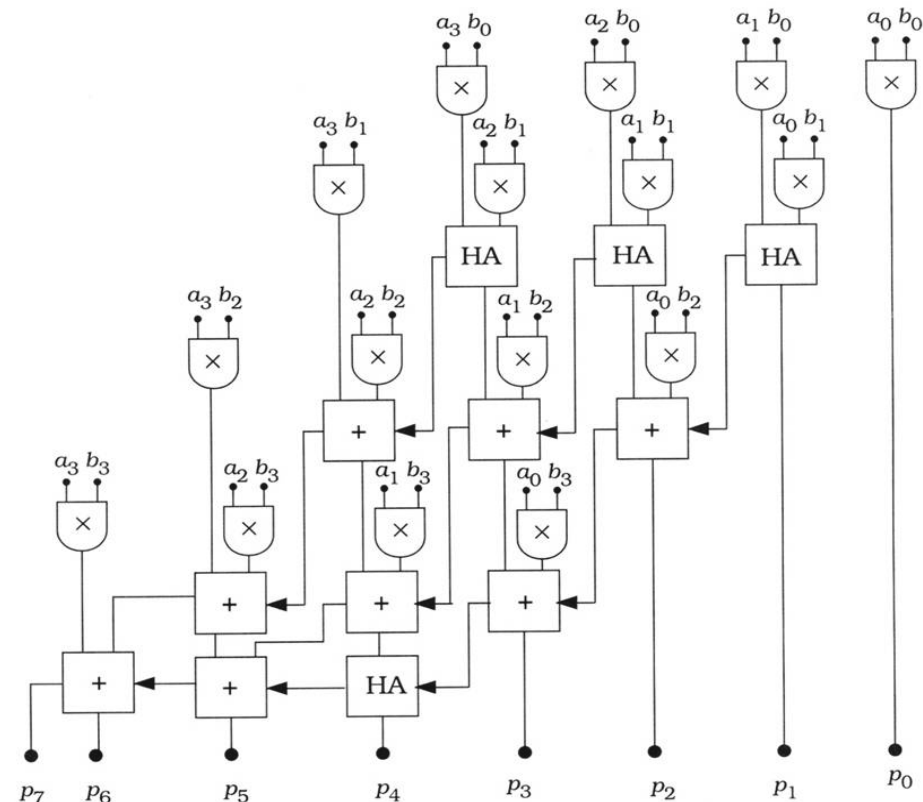


Figure 12.48 Details for a 4 X 4 array multiplier

Other Multipliers

 


Figure 12.49 Clocked input registers

b_{2k+1}	b_{2k}	b_{2k-1}	E_k	Effect on sum
0	0	0	0	add 0
0	0	1	+1	add A
0	1	0	+1	add A
0	1	1	+2	shift A left, add
1	0	0	-2	take two's (A), shift left, add
1	0	1	-1	add two's (A)
1	1	0	-1	add two's (A)
1	1	1	0	add 0

Figure 12.51 Summary of Booth encoded digit operations

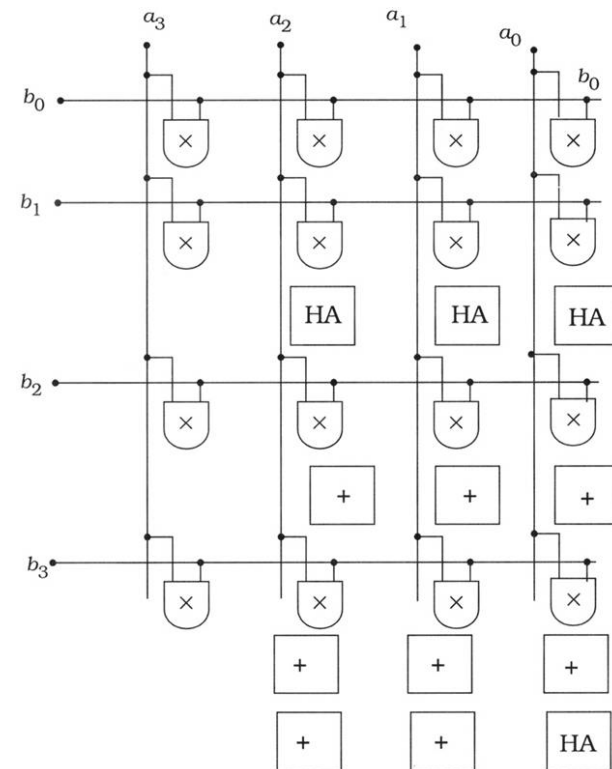


Figure 12.50 Initial cell placement for the array