



國立勤益科技大學


National Chin-Yi University of Technology

Introduction to VLSI Circuits and Systems

積體電路概論

Chapter 13

Memory and Programmable Logic

 

賴秉樑

Dept. of Electronic Engineering

National Chin-Yi University of Technology

Fall 2007

Outline

- ❑ The Static RAM
- ❑ SRAM Arrays
- ❑ Dynamic RAM
- ❑ ROM Arrays
- ❑ Logic Arrays

Static Random Access Memory, SRAM

- ❑ SRAM : cells use a simple bi-stable circuit to hold a data bit
 - » Three states: hold, write, and read operations
 - » Access transistors (NMOS) provide W/R operations



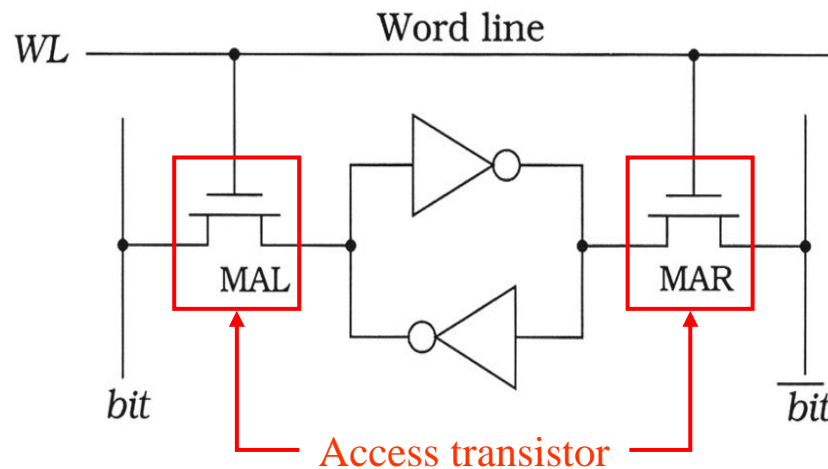


Figure 13.1 General SRAM cell

 

(a) 6T cell

 

(b) 4T cell with poly resistors

Figure 13.2 CMOS SRAM circuits

SRAM (1/2)


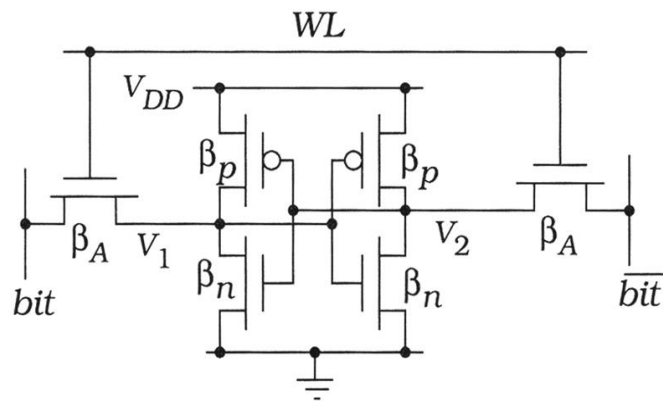


Figure 13.3 6T SRAM cell design parameters

 

(a) Write 1 operation

Write 1: in worst case,
 $V_1 = 0, V_2 = V_{DD}$
 $\rightarrow (\beta_A / \beta_n = 2)$
 Why??

$$\frac{(W/L)_{nA}}{(W/L)_n} \quad (13.1)$$


 


Figure 13.4 Butterfly plot

 Static Noise Margin: immunity
 the coupled electromagnetic
 signals (noise)



(b) Resistor model

Figure 13.5 Writing to an SRAM

SRAM (2/2)

 


Figure 13.6 Example of a basic 6-T SRAM cell layout

 


Figure 13.7 A 2-port CMOS SRAM cell

 


Figure 13.8 4-cell SRAM group

Outline

- ❑ The Static RAM
- ❑ SRAM Arrays
- ❑ Dynamic RAM
- ❑ ROM Arrays
- ❑ Logic Arrays

SRAM Arrays (1/4)

 


Figure 13.9 High-level view of an SRAM

 


Figure 13.10 Central SRAM block architecture

 


Figure 13.11 Cell arrangement in a core region

 


Figure 13.12 Row driver circuit

SRAM Arrays (2/4)

 


Figure 13.13 Column MUX/DeMUX network for 8-bit words

 


Figure 13.14 Logic 1 column driver

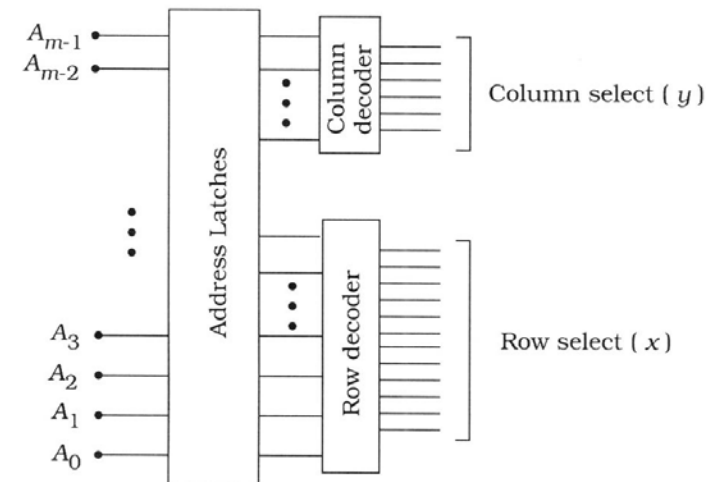


Figure 13.15 Basic addressing scheme

 


Figure 13.16 Address latch circuit

SRAM Arrays (3/4)

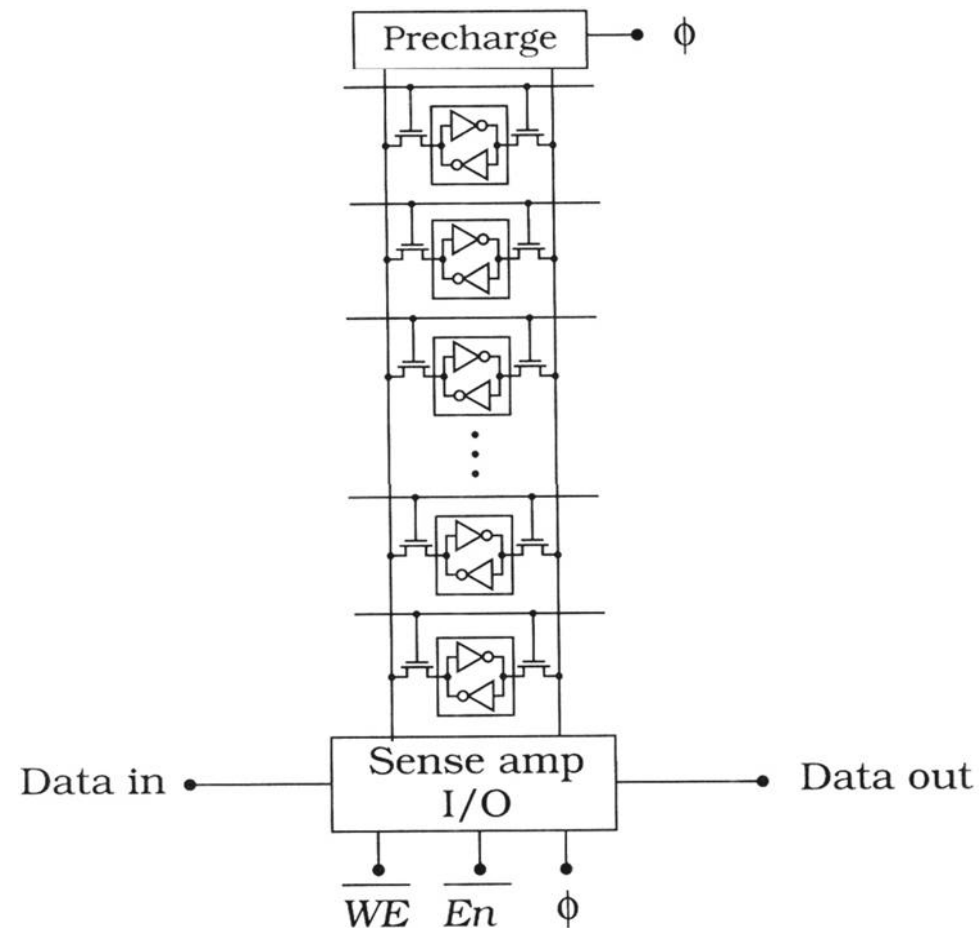


Figure 3.17 Pre-charge and I/O circuit for a single column

SRAM Arrays (4/4)

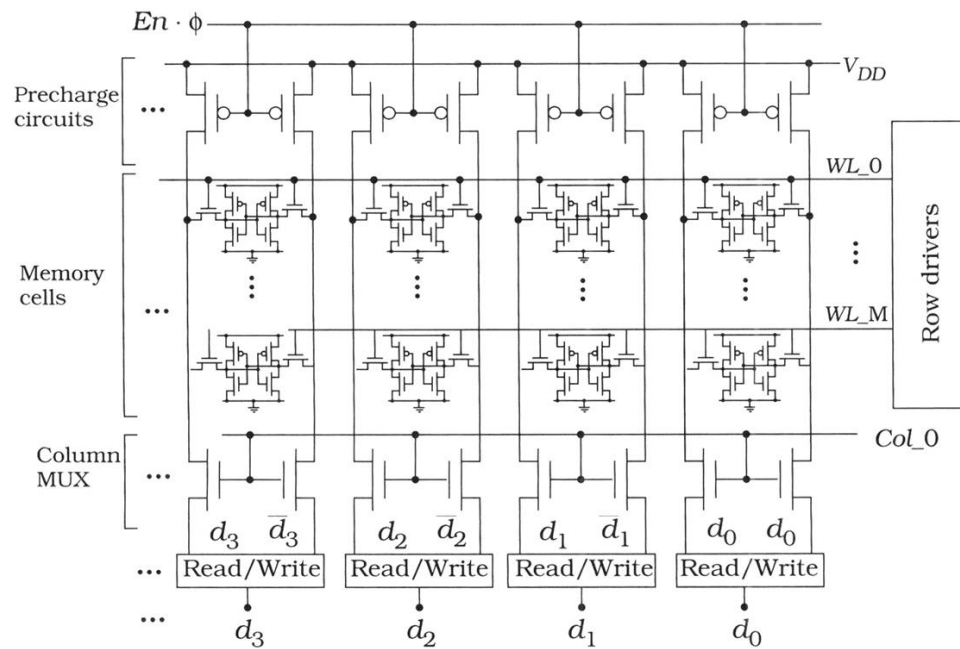


Figure 3.18 Expanded view of column circuitry

 


Figure 13.19 Write circuitry example

Sensing Operation


 


Figure 3.20 Example of a sensing scheme for the read operation

$$v_d = (v^+ - v^-) \quad (13.5)$$

$$v_{out} = Av_d = A(v^+ - v^-) \quad (13.6)$$
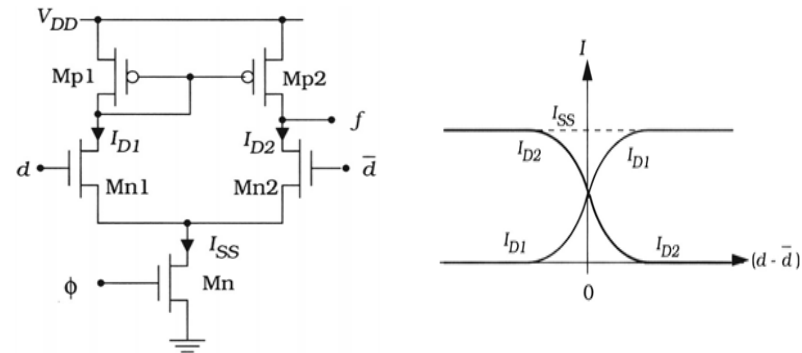
$$I_{SS} = I_{D1} + I_{D2} \quad (13.7)$$



(a) Circuit diagram

(b) Current flow

Figure 3.21 Single-ended differential amplifier


 


Figure 3.22 Dual-amplifier scheme for the sense amplifier network

An example: A Drowsy SRAM

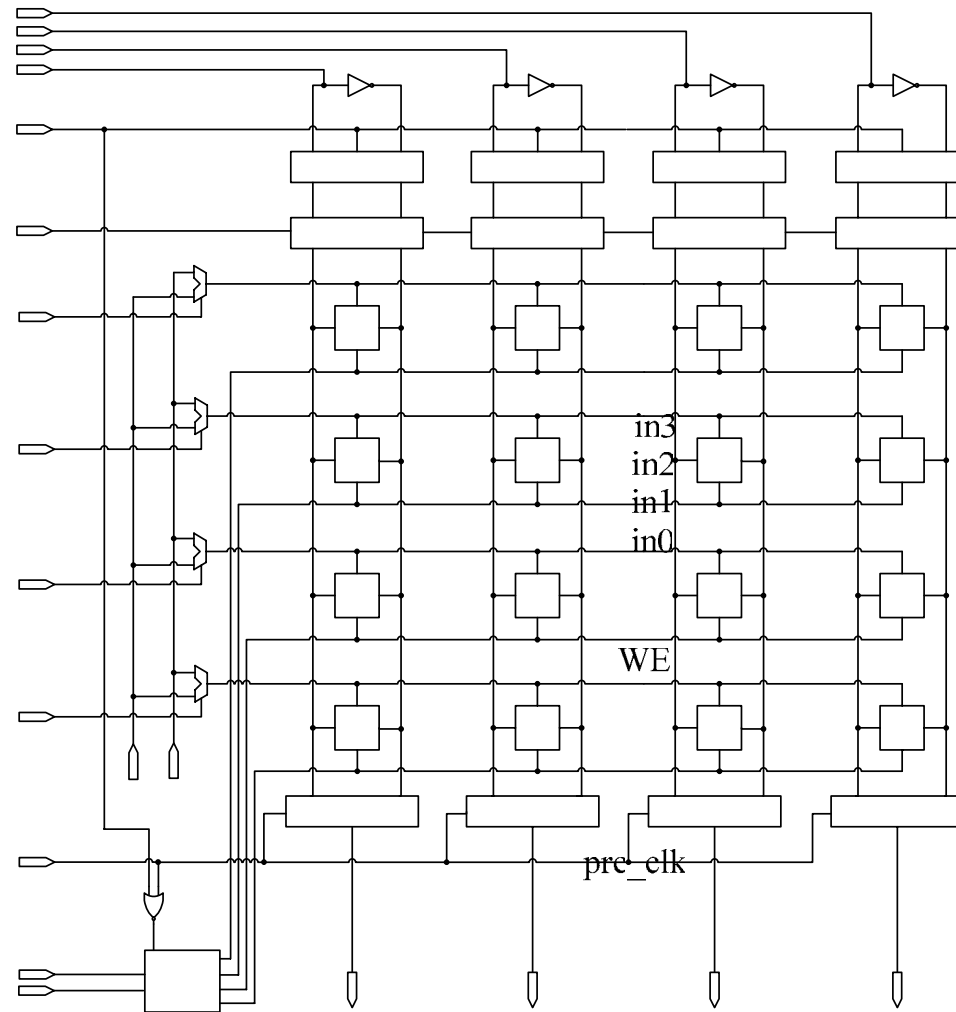

Write Circuit

BL0 BL0'

Precharge

V_{dd0}

Outline

- ❑ The Static RAM
- ❑ SRAM Arrays
- ❑ **Dynamic RAM**
- ❑ ROM Arrays
- ❑ Logic Arrays

DRAM (1/3)

❑ Dynamic RAM (DRAM)

- » Smaller than SRAM cells
- » Higher density storage arrays
- » As the central system memory in microcomputer systems
- » Require more peripheral circuitry

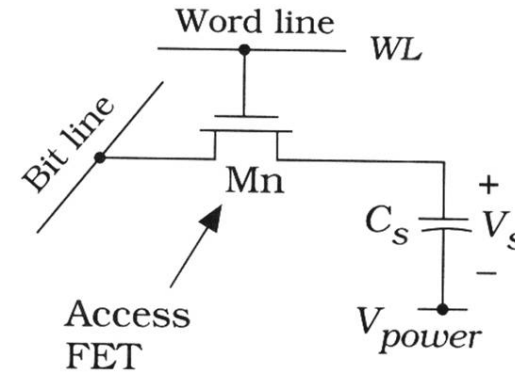



Figure 13.23 1T DRAM cell

$$Q_s = C_s V_s \quad (13.8)$$

For writing 1,

$$V_s = V_{\max} = V_{DD} - V_{Tn} \quad (13.9)$$
 
$$Q_{\max} = C_s (V_{DD} - V_{Tn}) \quad (13.10)$$



(a) Write operation

(b) Hold

Figure 3.24 Write and hold operations in a DRAM cell

DRAM (2/3)

- ❑ **Charge Leakage:** When $V_G < V_T$, a MOSFET is cutoff but still admits small leakage currents

$$I_L = -\left(\frac{dQ_s}{dt}\right) \quad (13.11)$$

$$I_L = -C_s \left(\frac{dV_s}{dt}\right) \quad (13.12)$$

$$I_L \approx -C_s \left(\frac{\Delta V_s}{\Delta t}\right) \quad (13.13)$$

$$t_h = |\Delta t| \approx \left(\frac{C_s}{I_L}\right)(\Delta V_s) \quad (13.14) \text{ (hold time or retention time)}$$

$$t_h = \left(\frac{50 \times 10^{-15}}{1 \times 10^{-9}}\right)(1) = 0.5 \mu s \quad (13.15) \text{ (} I_L=1 \text{ nA, } C_s=50 \text{ fF, and } V_s=1 \text{ V)}$$

$$f_{\text{refresh}} \approx \frac{1}{2t_h} \quad (13.16) \text{ (refresh frequency)}$$

 


Figure 3.25 Charge leakage in a DRAM cell

 


Figure 3.26 Refresh operation summary

DRAM (3/3)

 


Figure 3.26 Read operation in a DRAM cell

$$Q_s = C_s V_s \quad (13.17)$$

$$Q_s = C_s V_f + C_{bit} V_f \quad (13.18)$$

$$V_f = \left(\frac{C_s}{C_s + C_{bit}} \right) V_s \quad (13.19)$$

 


Figure 3.28 A DRAM cell using a trench capacitor


 


Figure 13.29 Visualization of stacked capacitor structure

DRAM Array and Peripheral Circuit

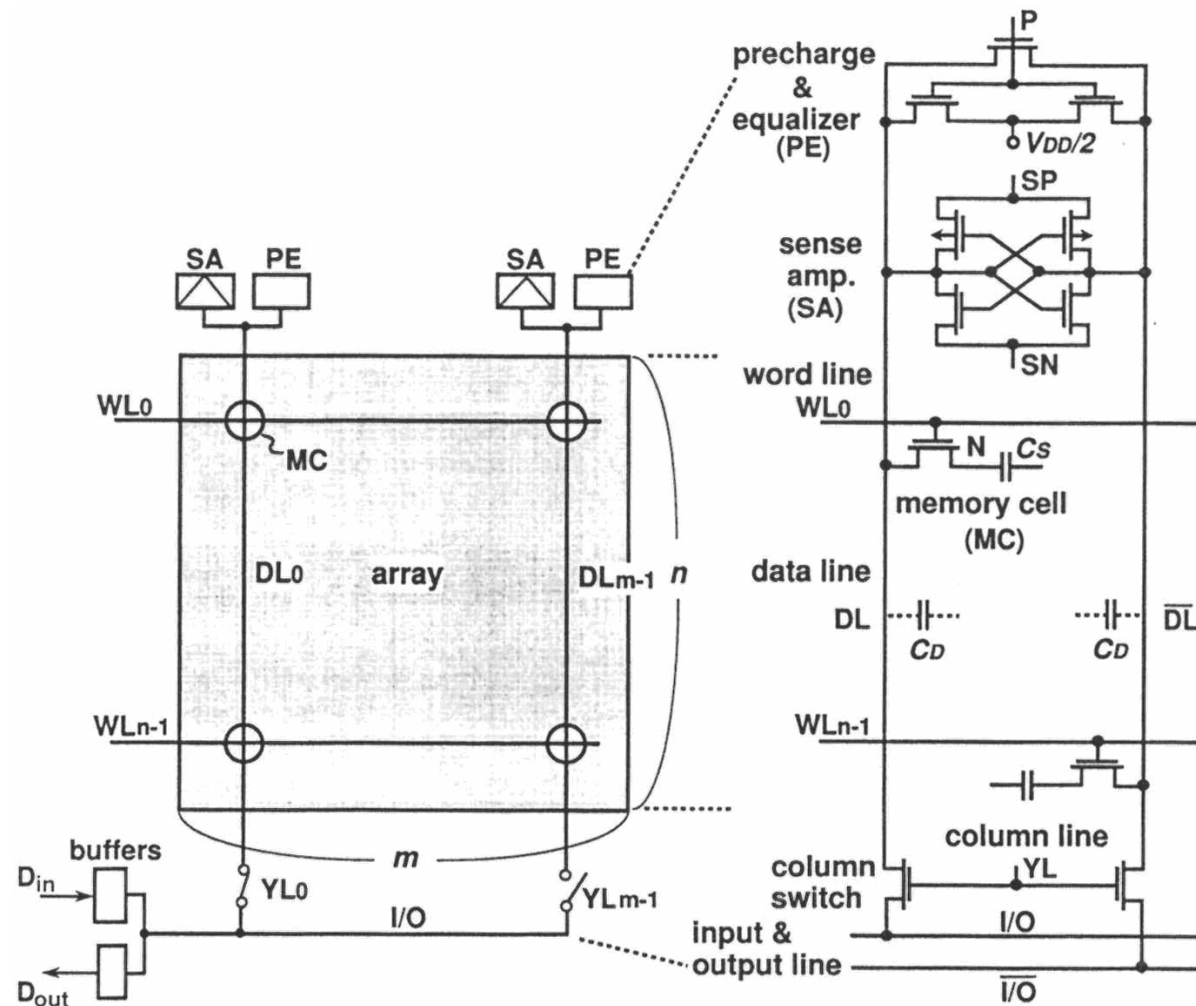

Divided-Word Line Architectures

 


Figure 13.30 Basic for a divided-word line architecture RAM layout

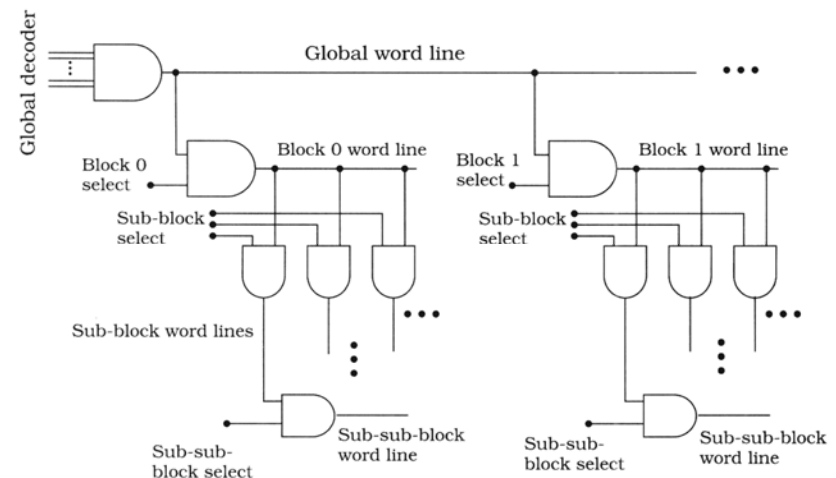


Figure 13.31 Logic for a DWL design

Outline

- ❑ The Static RAM
- ❑ SRAM Arrays
- ❑ Dynamic RAM
- ❑ ROM Arrays
- ❑ Logic Arrays

ROM

 


Figure 13.33 Logic diagram for a NOR-based ROM

 


Figure 13.35 Map for ROM layout

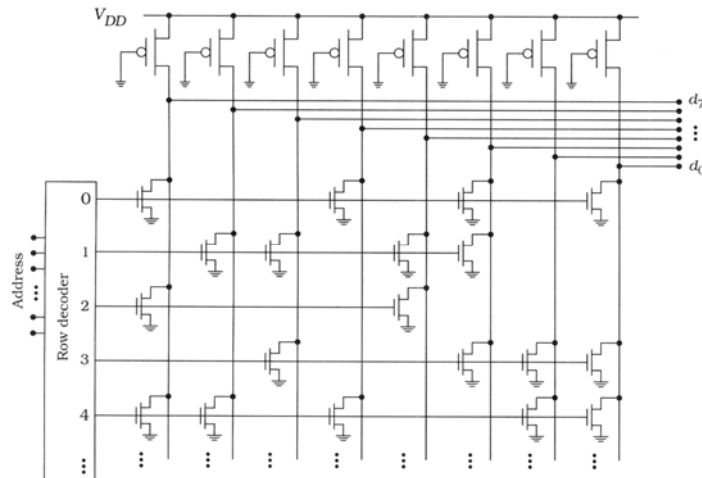


Figure 13.34 ROM array using pseudo-nMOS circuitry

 


Figure 13.36 ROM layout based on FET map

User-Programmable ROMs

- ❑ Electrically-erasable EPROMs (E²PROMs) are used to store the BIOS code in PC, and allow the user to update

 


Figure 13.37 Floating-gate MOSFET

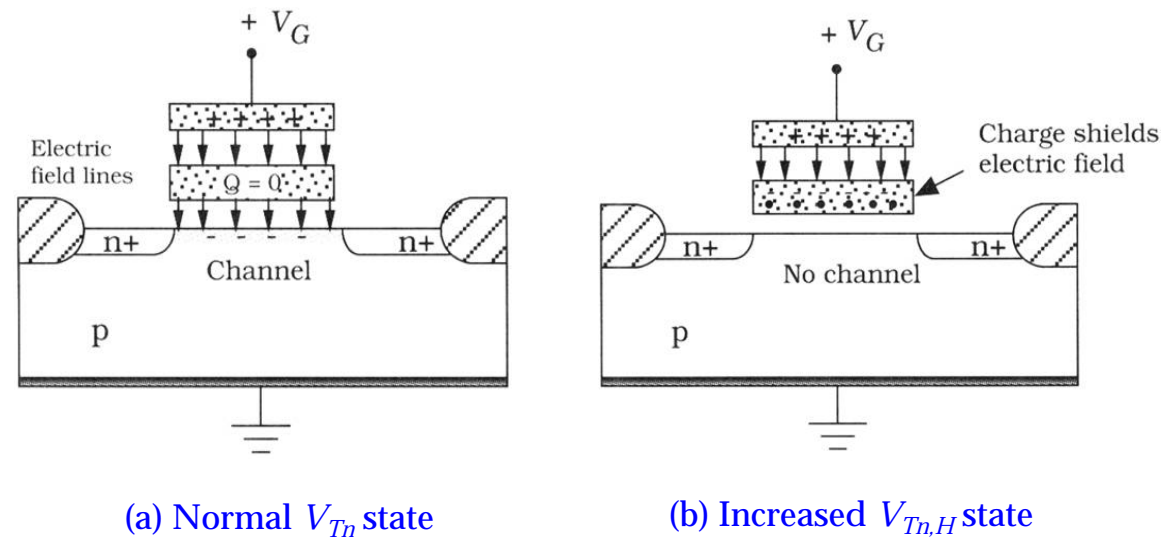


Figure 13.33 Logic diagram for a NOR-based ROM

E²PROMs

 


Figure 13.39 A E²PROM word using floating-gate nFETs

 


Figure 13.41 Fowler-Nordheim tunnelling

 


Figure 13.40 Programming a floating-gate FET

 


Figure 13.42 EEPROM cell with write line

Outline

- ❑ The Static RAM
- ❑ SRAM Arrays
- ❑ Dynamic RAM
- ❑ ROM Arrays
- ❑ Logic Arrays

Programmable Logic Array, PLA (1/2)

 


Figure 13.43 Structure of an AND-OR PLA



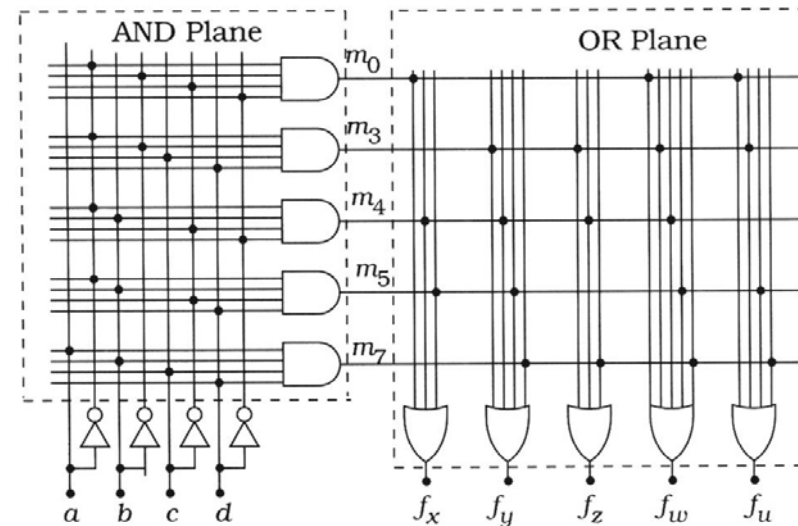


Figure 13.44 Logic gate diagram of the PLA

Programmable Logic Array, PLA (2/2)

 

(a) AND-OR logic

 

(b) NOR-based logic

Figure 13.45 NOR-gate PLA logic

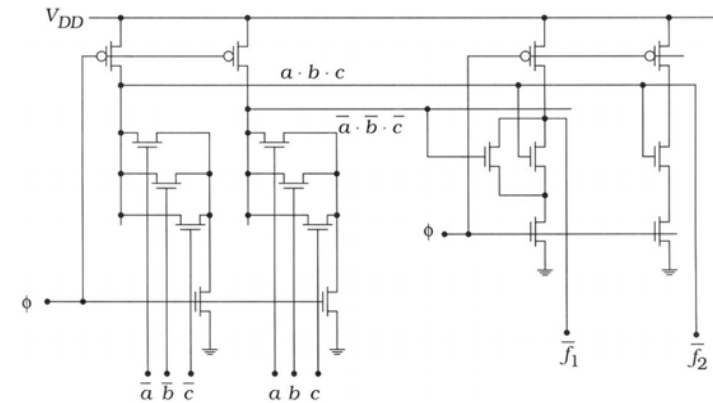


Figure 13.46 A dynamic CMOS PLA based on NOR gates



 


Figure 13.47 Generic NOR-based logic plane


Gate Array

 


(a) Gate array based

 


(b) NOR3 gate wiring

 

(a) Structure

 

(b) Metal-active

 

(c) Metal-metal

Figure 13.45 NOR-gate PLA logic

Figure 13.48 Transistor arrangement in a gate array