



國立勤益科技大學


National Chin-Yi University of Technology

Introduction to VLSI Circuits and Systems

積體電路概論

Chapter 10

System Specifications Using Verilog HDL

 

賴秉樑

Dept. of Electronic Engineering

National Chin-Yi University of Technology

Fall 2007

Reference textbook: “*Verilog HDL- A Guide to Digital Design and Synthesis*”, Samir Palnitkar

Introduction to VLSI Circuits and Systems, NCUT 2007

Outline

- ❑ Introduction
- ❑ Language Structure
- ❑ Modeling Part 1
- ❑ Modeling Part 2

Hardware Description Language

- ❑ Better be standard than be proprietary
- ❑ Can describe a design at some levels of abstraction
- ❑ Can be interpreted at many level of abstraction
 - » Cross functional, statistical behavioral, multi-cycles behavioral, RTL
- ❑ Can be used to document the complete system design tasks
 - » Testing, simulation, ..., related activities
- ❑ User define types, functions and packages
- ❑ Comprehensive and easy to learn

Verilog vs. VHDL

- ❑ Simulation Revenue (1995 first three quarters)
 - » Verilog: 51.84 millions (66.83: 1994)
 - » VHDL: 26.79 millions (59.23: 1994)
- ❑ ASIC Synthesis Revenue
 - » 97 millions on 1995 first three quarters
 - » 79.6 millions on 1994 first three quarters

HDL in Japan

- ❑ Around 15% of digital CMOS designers using HDL
- ❑ In ASIC market, 10-20% uses HDL and Synthesis
 - » Kanji Culture
- ❑ Two Years Behind USA
- ❑ A Verilog Stronghold

Design Methodologies

❑ Top-Down Design

- » Start with system specification
- » Decompose into subsystems, components, until indivisible
- » Realize the components

❑ Bottom-up Design

- » Start with available building blocks
- » Interconnect building blocks into subsystems, then system
- » Achieve a system with desired specification

❑ Meet in the middle

- » A combination of both

Verilog History


- ❑ Gateway Design Automation
 - » Phil Moorbr in 1984 and 1985
- ❑ Verilog-XL, “XL algorithm”, 1986
 - » Gate-level simulation
- ❑ Verilog logic synthesizer, Synopsis, 1988
 - » Top-down design methodology
- ❑ Cadence Design Systems acquired Gateway
 - » December 1989
 - » a proprietary HDL

Verilog History

- ❑ Open Verilog International (OVI), 1991
 - » Language Reference Manual (LRM)
- ❑ The IEEE 1364 working group, 1994
- ❑ Verilog become an IEEE standard (1364-1995)
 - » December, 1995
- ❑ 2001, IEEE standard 1364-2001

What is Verilog HDL?

 - ❑ Hardware description language
- ❑ Mixed level modeling
 - » Behavioral
 - Algorithmic
 - Register transfer
 - » Structural
 - Gate
 - Switch
- ❑ Single language for design and simulation
- ❑ Built-in primitives, logic function
- ❑ User-defined primitives
- ❑ Built-in data types
- ❑ High-level programming constructs



Basic unit (module)

- ❑ Module communication externally with input, output and bidirectional ports
- ❑ A module can be instantiated in another module

```
Module module_name(port_list);  
  declarations:  
    reg, wire, parameter, input, output, inout,  
    function, task  
  statements:  
    initial block  
    always block  
    module instantiation  
    gate instantiation  
    UDP instantiation  
    continuous assignment  
endmodule
```

Behavioral Modeling

- ❑ Procedural blocks
 - » **initial block:** executes only once
 - » **always block:** executes in a loop
- ❑ Block execution is triggered based on user-specified conditional
 - » **always @ (posedge clk)**
- ❑ All procedural blocks are automatically set at time 0 and execute concurrently
- ❑ **reg** is the main data type that is manipulated within a procedural block
 - » It holds its value until assigned a new value

An Example


```
Module FA_SEQ(A, B, CIN, SUM, COUT);  
    input A, B, CIN;  
    output SUM, COUT;  
    reg SUM, COUT;  
    reg T1, T2, T3;  
  
    always @ (A or B or CIN) /* at any time (A or B or CIN) changes */  
        begin /* when (A or B or CIN) changes, the block executes again */  
            // sequential execution  
            SUM = (A ^ B) ^ CIN;  
            T1 = A & CIN;  
            T2 = B & CIN;  
            T3 = A & B;  
            COUT = (T1 | T2) | T3;  
            // SUM, T1, T2, T3, COUT must be register data-type  
        end  
endmodule
```

Structural Modeling

- ❑ Gate-level design
 - » Built-in set of gate primitives interconnected by nets
and, nand, nor, ...
- ❑ Switch-level design
 - » Built-in switch-level primitives interconnected by nets nmos, ...
- ❑ Nets are continuously driven (like wires)

An Example
 
```
module FA_STR(A, B, CIN, SUM, COUT);  
  input A, B, CIN;  
  output SUM, COUT;  
  wire S1, S2, S3, S4, S5;  
  xor /* gate */  
    X1(S1, A, B),  
    X2(SUM, S1, CIN);  
  // X1, X2 are gate instantiation  
  and  
    A1(S2, A, B),  
    A2(S3, B, CIN),  
    A3(S4, A, CIN);  
  or  
    O1(S5, S2, S3),  
    O2(COUT, S4, S5);  
endmodule
```



Mixed Styles Modeling

- ❑ Structural and behavioral modelings can be freely mixed
- ❑ Values produced by procedural blocks can drive gates and switches
- ❑ Values from gates and switches can in turn be used with procedural blocks

An Example

```
module FA_MIX(A, B, CIN, SUM, COUT);  
  input A, B, CIN;  
  output SUM, COUT;  
  reg COUT;  
  reg T1, T2, T3;  
  
  wire S1;  
  
  xor X1(S1, A, B); // gate instantiation  
  
  always @ (A or B or CIN) // Always block  
  begin  
    T1 = A & CIN;  
    T2 = B & CIN;  
    T3 = A & B;  
    COUT = (T1 | T2 | T3);  
  end  
  assign SUM = S1 ^ CIN; // Continuous assignment  
endmodule
```


Description Styles

- ❑ Structural styles
 - » Gate level
 - » Structural Hierarchy
- ❑ Data Flow
- ❑ Behavioral styles
 - » Register Transfer Level
- ❑ Mixed


Gate Level Description Style

- ❑ Supports the following Verilog “gate type”
and, nand, or, nor,
xor, xnor, not
- ❑ The output or bidirectional terminals always come first in the terminal list, followed by the input terminals
For example:
nand N1 (Out1, In1, In2, In3, In4); // 4-input NAND
xor X1 (Out2, In5, In6); // 2-input XOR
- ❑ In the lowest level of modeling and so the real benefits of using a high level synthesis tool are not been exploited

Gate Level Description Style

□ Example 1: Half Adder
 
```
module HA (SUM, COUT, A, B);  
    input A, B;  
    output SUM, COUT;  
    xor XOR2 (SUM, A, B);  
    and AND2 (COUT, A, B);  
endmodule
```




Structural Hierarchy Description Style

- ❑ Direct instantiation and connection of models from a separate calling model to form structural hierarchy in a design
 - » Gate level
- ❑ A module may be declared anywhere in a design relative to where it is called
- ❑ Signals in the higher “calling” model are connected to signals in the lower “called” model by
 - » named association
 - » positional association

Structural Hierarchy Description Style

❑ Example 2: Full Adder
 
```
module FULL_ADD(A, B, CIN, SUM, COUT);  
  input A, B;  
  output SUM, COUT;  
  wire NET1, NET2, NET3;  
  HA U1 (NET1, NET2, B, CIN),  
    U2 (SUM, NET3, A, NET1);  
  OR2 U3 (COUT, NET2, NET3);  
endmodule
```



Structural Hierarchy Description Style

❑ Example 3: Decoder

```
module NAND3 (A, B, C, Y);
    input A, B, C;
    output Y;
    assign Y = !(A & B & C);
endmodule
module INV (A, Y);
    input A;
    output Y;
    assign Y = !A;
endmodule
```

```
module DECODER2X4 (Y, A, B, ENABLE);
    input A, B, ENABLE;
    output [3:0] Y;
    // N0 and N1 use positional associations
    NAND3 N0 (ABAR, BBAR, ENABLE, Y[0]);
           N1 (ABAR, B, ENABLE, Y[1]);
    // N2 and N3 use named associations
           N2 (.C(ENABLE),.Y(Y[2]),.B(BBAR),.A(A)),
           N3 (.B(B),.Y(Y[3]),.A(A),.C(ENABLE));
    INV I0 (A,ABAR), // positional
        I1 (.Y(BBAR),.A(B)); // named
endmodule
```

Data Flow Description Style

- ❑ Model combinational logic only
- ❑ Continuous signal assignments of type “wire” defined using the “assign” statement
- ❑ Continuous assignment statements are concurrent
- ❑ Right-hand side can be any function expression
- ❑ Left-hand side (target) can be a:
 - part-select
 - bit-select
 - concatenation of both
- ❑ Specified drive strengths and delays in an expression have no meaning to synthesis and are ignored

Data Flow Description Style

- ❑ Statements can take two forms:
 - » Explicit
 - » Specified in the declaration of the target wire

- ❑ Explicit

```
// declarations first
input [3:0] A, B;
input CIN;
output [3:0] SUM;
output COUT;
// theassignment
assign {COUT, SUM} = A + B + CIN;
```

- ❑ Specified in a wire declaration

```
// declaration and assignment combined
wire [3:0] parity = A ^ B;
```


Data Flow Description Style

□ Example 4: Half Adder

```
module HALF_ADD(SUM, COUT, A, B);  
    input A, B;  
    output SUM, COUT;  
    assign SUM = (A ^ B);  
    assign COUT = (A & B);  
endmodule
```

RTL Description Style

- ❑ Using the “always” block
- ❑ Can represent combinational logic, synchronous logic, or both
- ❑ Statements within a “always” block are sequential; their order of appearance is important
- ❑ Style of representation is very similar to C

❑ Example 5: Full Adder

```
module FULL_ADD (SUM, COUT, A, B, CIN);  
    input A, B, CIN;  
    output COUT, SUM;  
    reg COUT, SUM;  
    always @ (A or B or CIN)  
    begin  
        integer T1, T2, T3;  
        SUM = (A ^ B) ^ CIN;  
        T1 = A & CIN;  
        T2 = B & CIN;  
        T3 = A & B;  
        COUT = (T1 | T2) | T3;  
    end  
endmodule
```

Mixed Description Style

❑ Example 6: Full Adder

```
module FA_MIX (SUM, COUT, A, B, CIN);
    input A, B, CIN;
    output SUM, COUT;
    reg COUT;
    wire S1;
    XOR X1 (S1, A, B);
    always @ (A or B or CIN)
    begin
        integer T1, T2, T3;
        T1 = A & B;
        T2 = A & CIN;
        T3 = B & CIN;
        COUT = ( T1 | T2 ) | T3;
    end
    assign SUM = S1 ^ CIN;
endmodule
```

Simulation

- ❑ One language for design, stimulus, control, saving responses, and verification
 - » Stimulus and control
 - Use **initial** procedural block
 - » Saving responses
 - save on change
 - stored data
 - » Verification
 - automatic compares with expected responses

A Test Bench

```
module TOP;
  reg PA, PB, PCI;
  wire PCO, PSUM;
  // Instantiate module under test;
  FA_SEQ F1 (PA, PB, PCI, PSUM, PCO);
  // Positional.

  initial
  begin: ONLY_ONCE //block label
    reg [2:0] PAL; //3 bit vector
    for (PAL=0;PAL<8;PAL=PAL+1)
    begin
      {PA, PB, PCI} = PAL; //PA: MSB, PCI:LSM,
      #5 $display ("PA,PB,PCI=%b%b%b", PA, PB,
        PCI, " ::PCO,PSUM=%b%b", PCO,PSUM);
    end
    $stop;
  end
endmodule
```

statements executed sequentially

System-defined task

Delay 5ns after previous statement executed

Another Example

```

module RS_FF (Q, QBAR, R, S);
  output Q, QBAR;
  input R, S;
  nand #1 (Q, R, QBAR);
  nand #1 (QBAR, S, Q);
endmodule

```

1 time unit (ns) delay


```

module test;
  reg TS, TR;
  //Instantiate module under test;
  RS_FF INST_A (.Q(TQ), .QBAR(TQB), .S(TS), .R(TR));
  // Using name association.
initial
  TR = 0; TS = 0;
  #5 TS = 1;
  #5 TS = 0; TR = 1;
end

```

not defined
implicitly defined, one

Connect TQ to Q

 

```
#5 TS = 1; TR = 0;
#5 TS = 0;
#5 TR = 1;
#5 $stop;
end

// Display output;
initial
    $monitor ("At time %t," $time, "TR=%b, TS=%b, TQ=%b, TQB=%b",
              TR, TS, TQ, TQB);
endmodule
```

System-defined task

Outline

- Introduction
- Language Structure
- Modeling Part 1
- Modeling Part 2

Language Elements

Basics

- ❑ Free format
- ❑ Case sensitive
- ❑ white space (blank, tab, newline) can be used freely
- ❑ Identifiers: sequence of letters, \$ and _(underscore). First has to be a letter or an _
 - Symbol
 - symbol
 - _R2
 - R12_3\$
- ❑ Escaped identifiers: starts with a \ (backslash) and end with white space
 - \7400
 - \.*.\$
 - \.*}
 - \~Q
- ❑ Keywords: Cannot be used as identifiers
 - E.g. **initial**, **assign**, **module**

Basics (Contd)

- ❑ Comments: Two forms

- /* First form: can

- extend over

- many lines */

- // Second form: ends at the end of this line

- ❑ \$SystemTask / \$SystemFunction

- \$time**

- \$monitor**

- ❑ Compiler-directive: directive remains in effect through the rest of compilation.

- // Text substitution

- 'define MAX_BUS_SIZE 32

-

- reg['MAX_BUS_SIZE-1:0] ADDRESS;

Integer Numbers

- ❑ Integers: Decimal, hexadecimal, octal, binary

- ❑ Simple decimal form:

32 decimal 32
-15 decimal -15

- » Signed integers
- » Negative numbers are in two's complement form

- ❑ Base format form:

[<size>] '<base><value>

'hAF (h, A, F are case insensitive) // 8-bit hex

'o721 // 9-bit octal

5'O37 // 5-bit octal

4'D2 // 4-bit decimal

4'B1x02 // 4-bit binary

7'hx (x is case insensitive) // 7-bit x (x extended)

4'hz // 4-bit z (z extended)

-
- » Unsigned integers
 - » Padding:
 - 10'b10 // padded with 0's
 - 10'bx10 // padded with x's
 - » ? can replace z in a number: used to enhance readability where z is a high impedance

❑ _(underscore) can be used anywhere to enhance readability, except as the first character

❑ Example:

8'd-6 // illegal
-8'd6 // -6 held in 8 bits

Real Numbers

- ❑ Decimal notation

10.5

1.41421

0.01

- ❑ Scientific notation

23_5.1e2 (e is case insensitive) // 23510.0

3.6E2 // 360.0

5E-4 // 0.0005

- ❑ Must have at least one digit on either side of decimal

- ❑ Stored and manipulated in double precision (usually 64 bits)

Strings

- ❑ “Sequence of characters”
- ❑ `\n, \t, \\, \", %%`
 - `\n` = newline
 - `\t` = tab
 - `\\` = backslash
 - `\"` = quote mark (“)
 - `%%` = % sign

Value Set

- ❑ 0: logic-0 / FALSE
- ❑ 1: logic-1 / TRUE
- ❑ x: unknown / don't care, can be 0, 1, or z
- ❑ z: high-impedence

Data Types

❑ Nets

- » Connects between structural elements
- » Value is that of its drivers such as a continuous assignment or a gate
- » If no drivers connected to net, default value is z

wire [MSB:LSB] DAT; // vector wire

wire RDY, START;

wire [2:0] ADDR;

❑ Registers

- » Represent abstract data storage elements
- » Manipulated within procedural blocks
- » Value is saved from one assignment to the next
- » Default value is x

reg A, B, C; // 1-bit scalars

reg [-3:3] STRANGE;

reg [0:7] QBUS;

Net Types

- ❑ **wire, tri:** standard net
- ❑ **wor, trior:** wired-or net
- ❑ **wand, triand:** wired-and net
- ❑ **triereg:** capacitive (if all drivers at z, previous value is retained)
- ❑ **tri1:** pull up (if no driver, 1)
- ❑ **tri0:** pull down (if no driver, 0)
- ❑ **supply0:** ground
- ❑ **supply1:** power
- ❑ A net that is not declared defaults to a 1-bit wire

wire reset;

wor [7:0] DBUS;

supply0 GND;

wire [3:2] CLA, PLA;

tri [0:15] ABUS;

tri0 [-3:3] GND_BUS;

Register Types

- ❑ **reg**: any size, unsigned
- ❑ **integer**: 32-bit signed (2's complement)
- ❑ **time**: 64-bit unsigned
- ❑ **real, realtime**: 64-bit real number, defaults to an initial value of 0
- ❑ Examples:

reg CNT;

reg [31:0] WORD;

integer A, B, C; // 32-bit

integer HIST[2:6];

real [3:2] f, d;

realtime CURR_TIME;

time mark [0:15];

Parameters

- ❑ Constants
- ❑ Can be modified at compilation time (using **defparam** statement or in the module instance)
- ❑ Examples:
 - parameter** LINE_LENGTH = 132, X_S = 16'bx;
 - parameter** BIT = 1, BYTE = 8, PI = 3.14;
 - parameter** MID = (BYTE + BIT) / 2;
 - parameter** TEST_FILE = "/home/bhasker/TEST/testfile";
- ❑ Common uses: to specify delays and widths

Memories

- ❑ Array of integers

- ❑ No multiple dimensions

```
reg [0:3] MY_MEM [0:63];    // 64 s-bit registers
```

- ❑ Entire memory cannot be assigned a value in a single assignment

```
reg [1:3] A; // 3-bit register, A=000
```

```
reg B [1:3]; // 3 1-bit registers, {B[1], B[2], B[3]}=000
```

- ❑ Can load memory by using a system mask:

```
$readmem<base>("<filename>",<memory_name>,<start>,<finish>);
```

<base> is b or h

Gate-Level Modeling

Primitive Gates

- ❑ Built-in

- ❑ **and, nand, or, nor, xor, xnor**

 - » First terminal is output, followed by inputs

 - wire** a1 (out1, in1, in2);

 - nand** a2 (out2, in21, in22, in23, in24);

- ❑ **buf, not**

 - » One or more outputs first, followed by one input

 - not** N1 (no1, no2, no3, no4, nin);

 - buf** B1 (bo, bin);

- ❑ **bufif0, bufif1, notif0, notif1: tree-state drivers**

 - » Output terminal first, then input, then control

 - bufif1** BF1 (outb, inb, ctrlb);

Primitive Gates

- ❑ **pullup, pulldown**

- » Put 1 or 0 on all terminals

- pullup** PUP (pu1, pu2, pu3);

- ❑ Instance names are optional

- not** (XBAR, X);

Delays

- ❑ Signal propagation delay from any gate input to the gate output
- ❑ Up to three values per output: rise, fall, turn-off delay

```
not N1 (XBAR, X);           // Zero delay
nand #(6) (out, in1, in2);  // All delays = 6
and #(3,5) (out, in1, in2, in3); /* rise delay = 3, fall delay = 5,
                                   to_x_or_z = min(3,5) */
```

- ❑ Each delay can be written in *min:typ:max* form as well

```
nand #(2:3:4, 4:3:4) (out, in1, in2);
```
- ❑ Can also use a specify block to specify delays

Time Unit and Precision

- ❑ Compiler directive: **'timescale**

'timescale *time_unit* / *time_precision*;

- ❑ 1, 10, 100 /s, ms, us, ns, ps, fs

'timescale 1ns / 100ps

module AND_FUNC (Z, A, B);

output Z;

input A, B;

and # (5.22, 6.17) A1 (Z, A, B);

endmodule

/* Delays are in ns. Delays are rounded to one-tenth of a ns (100ps). Therefore,

5.22 becomes 5.2ns, 6.17 becomes 6.2ns and 8.59 becomes 8.6ns */

// If the following timescale directive is used:

'timescale 10ns / 1ns

// Then 5.22 becomes 52ns, 6.17 becomes 62ns, 8.59 becomes 86ns

Delay Scaling

- ❑ The **'timescale** directive specifies the units and precision for all delay values in all modules that follow this directive until another **'timescale** directive or reset is found

```
'timescale 1ns / 100ps
module AND_FUNC (Z, A, B);
    output Z;
    input A, B;
    and # (5.22, 6.17) A1 (Z, A, B);
endmodule

'timescale 10ns / 1ns
module TB;
    reg PUT_A, PUT_B;
    initial begin
        PUT_A=0; PUT_B=0;
        #5.21 PUT_B=1;
        #10.6 PUT_A=1;
        #15 PUT_B=0;
        #20 $finish;
    end
    AND_FUNC AF1 (GET_0, PUT_A, PUT_B);
endmodule
```

-
- ❑ Simulation always take place in smallest time precision, which is 100ps in the above example
 - ❑ In module TB, delays are scales to 100ps. For example, 1 is applied to PUT_B at 520 hundred ps.

Getting Simulation Time

- ❑ System function, **\$time**: returns the simulation time as an integer value scaled time unit specified.

```
'timescale 10ns / 1ns
module TB;
    .....
    initial
        $monitor ("PUT_A=%d PUT_B=%d", PUT_A, PUT_B,
            "GET_O=%d", GET_O, "at time %t", $time);
endmodule

PUT_A=0 PUT_B=0 GET_O=0 at time 0
PUT_A=0 PUT_B=1 GET_O=0 at time 5
PUT_A=0 PUT_B=0 GET_O=0 at time 11
.....
/* $time value is scaled to the time unit and then rounded */
```

-
-
- ❑ System function, **\$realtime**: returns the simulation time as a real number scaled time unit.

```
'timescale 10ns / 1ns
module TB;
    .....
    initial
        $monitor ("PUT_A=%d PUT_B=%d", PUT_A, PUT_B,
            "GET_O=%d", GET_O, "at time %t", $realtime);
endmodule

.....
PUT_A=0 PUT_B=1 GET_O=0 at time 5.2
PUT_A=0 PUT_B=0 GET_O=0 at time 10.6
```

Array of Instances

- ❑ An array of instances can be specified using the range specification

```
wire [3:0] OUT, INA, INB;
```

```
.....
```

```
nand NG [3:0] (OUT, INA, INB);
```


```
// This is the same as:
```

```
nand  NG3 (OUT[3], INA[3], INB[3]),  
      NG2 (OUT[2], INA[2], INB[2]),  
      NG1 (OUT[1], INA[1], INB[1]),  
      NG0 (OUT[0], INA[0], INB[0]);
```

Array of Instances

❑ 4x1 multiplexer circuit
 
```
module MUX4x1 (Z, D0, D1, D2, D3, S0, S1);  
  output Z;  
  input D0, D1, D2, D3, S0, S1;  
  
  and (T0, D0, S0BAR, S1BAR),  
      (T1, D1, S0BAR, S1),  
      (T2, D2, S0, S1BAR),  
      (T3, D3, S0, S1);  
  
  not (S0BAR, S0),  
      (S1BAR, S1);  
  
  or (Z, T0, T1, T2, T3);  
endmodule
```



A Clock Generator

```
module CLOCK (CLK);  
    output CLK;  
  
    initial begin  
        START = 1;  
        #3 START = 0;  
    end  
  
    nor #5 (CLK, START, CLK);  
endmodule  
  
// Generate a clock with on-off width of 5  
// Not synthesizable  
// For waveform only
```

Implicit nets

- ❑ If a net is not declared, it is assumed to be a single bit wire
- ❑ Compiler directive to override:

'default_nettype *net_type*

// Example:

'default_nettype wand

- ❑ Directive occurs outside of module. Stays in effect until next same directive is reached or reset.

Printing Values

- ❑ **\$display** system task: Prints the specified list of arguments to output and adds a newline automatically.

\$display | **\$displayb** | **\$displayh** | **\$displayo**

(*arg1, arg2,, argN*);

// Example:

\$display ("Simulation time is %t", \$time);

\$display (\$time, "R=%b, S=%b, Q=%b, QB=%b", R, S, Q, QB);

- ❑ **\$monitor** system task: Task us called whenever a change occurs in argument list.

initial


\$ monitor ("At %d, d=%d, clk=%d", \$time, d, clk, "and q is %b", q);

» Only one monitor can be active at any time

\$ monitoroff // Disable all monitors;

\$ monitoron // Enable all monitors;

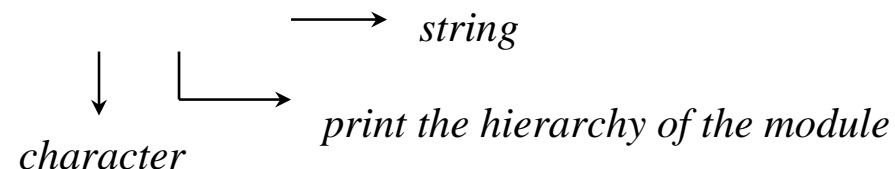- ❑ Formatting chars.: %h, %d, %o, %b, %c, %m, %s



User-Defined Primitives

Basics


- ❑ Arguments the set of predefined gate primitives.
- ❑ Use exactly the same way as gate primitives.
- ❑ May be a combinational UDP or a sequential UDP.
- ❑ A sequential UDP may model both level-sensitive and edge-sensitive behavior.
- ❑ Behavior is described as a table.
- ❑ Acceleratable.
- ❑ Each UDP has one output: 0, 1, x (z is not allowed).
- ❑ If input is z, it becomes an x.
- ❑ In a sequential UDP, output has the same value as the internal state.

Combinational UDP

```
primitive MUX1BIT (Z, A, B, SEL);
  output Z;
  input A, B, SEL;

  table
    //  A    B    SEL    :    Z
    0    ?    1    :    0
    1    ?    1    :    1
    ?    0    0    :    0
    ?    1    0    :    1
    0    0    x    :    0
    1    1    x    :    1
  endtable
endprimitive
```

Don't care

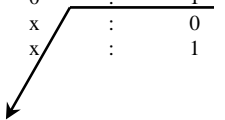

- ❑ Any combination that is not specified is an x.
- ❑ Output port must be the first port.
- ❑ “?” represents iteration over “0”, “1”, or “x” logic values

Sequential UDP (Level)

- ❑ Level-sensitive sequential UDP example:

```
primitive LATCH (Q, CLK, D);
```

```
    output Q;
```

```
    reg Q;
```

```
    input CLK, D;
```

```
    table
```

//	CLK	Data		State		Output(next state)
1	1	:	?	:	1	;
1	0	:	?	:	0	;
0	?	:	?	:	-	;

```
    endtable
```

```
Endprimitive
```

- ❑ “?” means don’t-care
- ❑ “-” means no change in output

Sequential UDP (Edge)

- ❑ Edge-sensitive sequential UDP example:

```
primitive D_EDGE_FF (Q, CLK, D);
```

```
  output Q;
```

```
  reg Q;
```

```
  input CLK, D;
```

```
  table
```

```
    // CLK Data      State      Output(next state)
```

```
    (01) 0   :   ?   :   0       ;
```

```
    (01) 1   :   ?   :   1       ;
```

```
    (0x) 1   :   1   :   1       ;
```

```
    (0x) 0   :   0   :   0       ;
```

```
    // Ignore negative edge of clock;
```

```
    (?0) ?   :   ?   :   -       ;
```

```
    // Ignore data change on steady clock;
```

```
    ?    (??) :   ?   :   -       ;
```

```
  endtable
```

```
endprimitive
```

Continuous Assignments

Basics

- ❑ Models behavior of combinational logic
- ❑ Dataflow style
- ❑ Assign a value to a net
- ❑ Examples:

```
wire [3:0] Z, PRESET, CLEAR;  
assign Z = PRESET & CLEAR;
```

```
wire COUT, CIN;  
wire [3:0] SUM, A, B;  
assign {COUT, SUM} = A + B + CIN;  
assign MUX = (S == 0) ? A: 'bz,  
          MUX = (S == 1) ? B: 'bz,  
          MUX = (S == 2) ? C: 'bz,  
          MUX = (S == 3) ? D: 'bz;  
assign Z = ~(A | B) & (C | D);
```

- ❑ Expression on right-hand side is evaluated whenever any operand changes

Net Declaration

- ❑ Can have an assignment in the net declaration

```
wire [3:0] A = 4'b0;  
assign PRESET = 'b1;
```

```
wire #10 A_GT_B = A > B;
```

- ❑ Only one assignment to a net using net declaration
- ❑ Multiple assignments to a net is done using continuous assignments

Delay

- ❑ Delay between assignment of right-hand side to left-hand side

wire #10 A = B && C; // Continuous delay

- ❑ Net delay

wire #10 A;

// Any change to A is delayed 10 time units before it takes effect

- ❑ If delay is in a net declaration assignment, then delay is not net delay

wire #10 A = B + C;

// 10 time units is part of the continuous assignment and not net delay

- ❑ If value changes before it has a chance to propagate, latest value change will be applied

» Inertial delay

Operands

1. Numbered operands

2. Functional call operands

- » A functional call can be used as an operand within an expression

```
wire [7:0] A;  
// PARITY is a function described elsewhere  
assign PAR_OUT = PARITY(A);
```

3. Bit selects

```
input [3:0] A, B, C;  
output [3:0] SUM;  
assign SUM[0] = (A[0] ^ B[0] ^ C[0]);
```

4. Part selects

5. Memory addressing

```
reg [7:0] RegFile [0:10];    // 11 b-bit registers  
reg [7:0] A;  
RegFile[3] = A;              // A assigned to 3rd register in RegFile
```

Operators

1. Arithmetic
2. Relational
3. Equality
4. Logical
5. Bit-wise
6. Reduction
7. Shift
8. Conditional
9. Concatenation

Arithmetic Operators

+	(plus)
-	(minus)
*	(multiply)
/	(divide)
%	(modulus)

- ❑ Integer division will truncate
- ❑ % gives the remainder with the sign of the first operand
- ❑ If any bit of operand is **x** or **z**, the result is **x**
- ❑ *reg* data type holds an unsigned value, while *integer* data type holds a signed value

```
reg [0:7] A;  
integer B;  
A = -4'd6;      // reg A has value unsigned 10  
B = -4'd6;      // integer B has value signed -6  
A-2            // result is 8  
B-2            // result is -8
```

Relational Operators

>	(greater than)
<	(less than)
>=	(greater than or equal to)
<=	(less than or equal to)

- ❑ If there are x or z in operand, the result is x
- ❑ If unequal bit lengths, smaller operand is zero-filled on most significant side (I.e., on left)

Equality Operators

<code>==</code>	(logical equality, result may be unknown)
<code>!=</code>	(logical inequality, result may be unknown)
<code>===</code>	(case equality, x and z also compared)
<code>!==</code>	(case inequality, x and z also compared)

`A = 'b11x0;`

`B = 'b11x0;`

`A == B` is known.

`A === B` is true

- ❑ Unknown is same as false in synthesis
- ❑ Compare bit by bit, zero-filling on most significant side

Logical Operators

&& (logical and)

|| (logical or)

A = 'b0110; // non-zero

B = 'b0100; // non-zero

A || B is 1.

A && B is also 1

- ❑ Non-zero value is treated as 1
- ❑ If result is ambiguous, set it to x

Bit-wise Operators

~	(unary negation)
&	(binary and)
	(binary or)
^	(binary exclusive-or)
~^, ^~	(binary exclusive-nor)

A = 'b0110;

B = 'b0100;

A | B is 0110

A & B is 0100

- ❑ If operand sizes are unequal, smaller is zero-filled in the most significant bit side

Reduction Operators

&	(unary and)
~&	(unary nand)
	(unary or)
~	(unary nor)
^	(unary xor)
~^	(unary xnor)

A = 'b0110;
B = 'b0100;

| B is 1

& B is 0

- Bitwise operation on a single operand to produce 1-bit result

Shift Operators

<< (left shift)
>> (right shift)

reg [0:7] D;

D = 4'b0111;

D >> 2 has the value 0001

- ❑ Logic shift, fill vacant bits with 0
- ❑ If right operand is an x or a z, result is x
- ❑ Right operand is always an unsigned number

Conditional Operators

expr1 ? expr2:expr3

wire [0:2] GRADE = SCORE > 60 ? PASS:FAIL;

- If *expr1* is an x or a z, *expr2* and *expr3* are combined bit by bit (all x's except 0 with 0 = 0, 1 with 1 = 1)

Concatenation and Replication

```
wire [7:0] DBUS;
```

```
wire [11:0] ABUS;
```

```
assign ABUS[7:4] = {DBUS[0], DBUS[1], DBUS[2], DBUS[3]};
```

```
assign ABUS = {DBUS[3:0], DBUS[7:4]};
```

```
assign DBUS[7:4] = {2{4'B1011}}; // 1011_1011
```

```
assign ABUS[7:4] = {{4{DBUS[7]}}, DBUS}; // sign extension
```

Outline

- ❑ Introduction
- ❑ Language Structure
- ❑ Modeling Part 1
- ❑ Modeling Part 2

Behavioral Modeling

Procedure Blocks

- ❑ Use procedural blocks to describe the operation of the circuit
- ❑ Two procedural blocks:
 - » *always* block: executes repetitively
 - » *initial* block: executes once
- ❑ Concurrent procedural blocks
- ❑ All execute concurrently
- ❑ All activated at time 0

An Example

```
module TWO_PHASE;  
    reg PH_A, PH_B;  
  
    initial  
    begin  
        PH_A = 'b0;  
        PH_B = 'b1;  
    end  
  
    always  
    begin  
        #10 PHA_A = ~PH_A;  
    end  
  
    always  
    begin  
        #15 PHA_B = ~PH_B;  
    end  
endmodule
```

Another Example

```
reg [0:5] instr_reg;
reg [3:0] accum;
wire execute_cycle;

always @(execute_cycle)
begin
    case (instr_reg{0:1})
        2'b00 : STORE (accum,instr_reg[2:5]);
        2'b01 : LOAD (accum,instr_reg[2:5]);
        2'b10 : JUMP (instr_reg[2:5]);
        2'b11 ;;
    endcase
end
// STORE, LOAD, and JUMP are user defined tasks
```

The *always* Block

Can model:

- » combinational logic
- » sequential logic

Syntax:

```
// Single statement
always @ (event expression)
    statement
```

```
// Sequential statement
always @ (event expression)
    begin
        sequential statements
    end
```

The *always* Block

- » “event expression” specified a set of events based on which statements within the always block are executed sequentially
- » The type of logic synthesized is based on what is specified in the “event expression”
- » Four forms of event expressions are supported
 - An OR of several identifiers (comb/seq logic)
 - The rising edge clock (register inference)
 - The falling edge clock (register inference)
 - Asynchronous reset (register inference)

Event Expressions

1. An OR of several identifiers

- » Combinational or synchronous logic may be represented by a set of sequential statements

```
always @ (id1 or id2 or id3 or ... or idn)
```

```
begin
```

```
    sequential_statements
```

```
end
```

- ❑ A synchronous block may appear inside an always block (representing synchronous logic) in two forms:

```
always @ (posedge clock_name)
```

```
begin
```

```
    sequential_statements
```

```
end
```

```
always @ (negedge clock_name)
```

```
begin
```

```
    sequential_statements
```

```
end
```

- ❑ Sequential statements not within a sequential block represents combinational logic

Example:

```
module Comb (A, B, C, Y);  
  input A, B, C;  
  output Y;  
  reg Y;  
  
  always @ (A or B or C)  
  begin  
    Y = A ^ B ^ C;  
  end  
endmodule
```


Event Expressions

2. The rising edge clock (register inference)

- » The event expression denotes the rising edge of a clock
- » The behavior within block represents synchronous logic triggered on the rising edge of clock

```
always @ (posedge CLK)
begin
    Q = D;
end
```


3. The falling edge clock (register inference)

- » The event expression denotes the falling edge of a clock
- » The behavior within block represents synchronous logic triggered on the falling edge of clock

```
always @ (negedge CLK)
begin
    Next_state = Current_state;
end
```

Register Inference
 
```
module SEQ (CLK, A, B, Y);  
  input CLK, A, B;  
  output Y;  
  reg Y;  
  
  always @ (posedge CLK)  
  begin  
    Y = A + B;  
  end  
endmodule
```



Event Expressions

4. Asynchronous reset (register inference)

- » Asynchronous resets in addition to register inferences (2 & 3 above)

always @ (negedge reset1 or posedge CLK or posedge reset2)

begin

if (!reset1)

begin

/* sequential_statements

asynchronous input triggered by the false condition of reset1 to the registers */

end

else

begin

/* sequential_statement

Optional for sequential statements. Could well have “else-if” clauses */

if (!reset2)

begin

/* sequential_statements: Asynchronous inputs triggered by reset2 */

end

else

begin

// sequential_statements: register inference statements.

end

end

end

Register Inference

- ❑ The language constructs “registers” is synthesized as a hardware register (flip-flop) if the register is assigned a value in:
 - » A sequential block
 - » An “always” block that has an event expression denoting a rising or falling clock edge
- ❑ It is illegal to assign a register value on both rising and falling edges of a clock

Sequential Statements and the Always Block

- ❑ Only “registers” and “integers” may be assigned values in sequential statements
- ❑ If an output port of the module is to be assigned a value in an always block it generally must be declared to be of a register type as well
- ❑ Possible sequential statements within an always block are
 - procedure assignment
 - synchronous block
 - if statement
 - case statement
 - for-loop statement
 - repeat loop statement
 - block statement
 - task enabling
- ❑ An “always” block is concurrent and so may appear in any order within a module body with other continuous assignments (module instantiations or other always block)
- ❑ Data is passed out of an always block using register variables

Procedural Assignments

- ❑ The assignment statements that can be used inside an always blocks
- ❑ Similar to continuous assignment statements except that the target must be a register or integer type
- ❑ The following forms are allowed as a target of a procedural assignment:
 - register variables
 - bit-select of register variables
 - part-select of register variables
 - concatenations of above
 - Integers
- ❑ Examples:
 - `A = B << 2;`
 - `CTRL = (opcode == 2'b01);`
 - `sum = a + b;`

Procedural Assignments

- ❑ Assignments are always processed bit-wise
- ❑ If the bit-width of an expression on the right-hand side is larger than that of the target, the extra bits are discarded
- ❑ If an expression's bit-width is less than that of the target, zeros are added at the left, or signed bits is extended for signed numbers
 - » Note that integers always hold signed numbers, while wires and registers always hold unsigned numbers

Blocking v.s. Non-Blocking

❑ Blocking (=)

- » Assignment are blocked, i.e., they must be executed before subsequent statements are executed

always @ (posedge clock)

begin

B = A;

C = B;

D = C;

end

- » 1 flip-flop (Data in is A, data out is D)

❑ Non-blocking (<=)

- » Assignment are not blocked, i.e., can be scheduled to occur without blocking the procedural flow

always @ (posedge clock)

begin

B <= A;

C <= B;

D <= C;

end

- » 3 pipelined flip-flops (A to B to C to D)

Blocking v.s. Non-Blocking

❑ Blocking procedural assignment:

- » Assignment is executed before any of the following ones are executed.
- » Only applies to its own sequential block.

```
reg_a = 10;
```

❑ Non-blocking procedural assignment.

- » The procedural flow is not blocked

```
# 2
```

```
reg_a <= LOAD;
```

```
reg_b <= STORE;
```

- » Evaluate right-hand side and schedules the assignment.
- » At the end of the current loop, assignment to the left-hand side is made

Examples

❑ Blocking assignment

```
initial
begin
    CLR = #5 0;
    CLR = #4 1;
    CLR = #10 1;
end
// CLR is assigned at time 5, and then at 9 and then at 19
```

delay between *RHS* and *LHS*

❑ Non-blocking assignment

```
initial
begin
    CLR <= #5 1;
    CLR <= #4 0;
    CLR <= #10 1;
end
// CLR is assigned 0 at time 4, 1 at time 5 and 1 at time 10
```

- » Value is indetermined if multiple values are assigned at the same time

Procedural Continuous Assignment

- ❑ Allow expression to be driven continuously into integers or nets
- ❑ *assign* and *deassign* procedural statements: for integers
- ❑ *force* and *release* procedural statements: for nets

Assign and Deassign

- ❑ An *assign* procedural statement overrides all procedural assignments to a register
- ❑ The *deassign* procedural statement ends the continuous assignment to a register
- ❑ Value remains until assigned again
- ❑ If assign applied to an already assigned register, it is deassigned first before making the new procedural continuous assignment

```
module DFF (D, CLR, CLK, PRESET, Q);
    input D, CLR, CLK, PRESET;
    output Q;
    reg Q;
    always @ (CLR or PRESET)
        if (!CLR)
            assign Q = 0; // D has no effect on Q
        else if (!PRESET)
            assign Q = 1; // D has no effect on Q
        else
            deassign Q;
    always @ (posedge CLK)
        Q = D;
endmodule;
```

Force and Release

- ❑ Similar to assign-deassign, except that it can be applied to nets as well as registers
- ❑ *force* procedural statement on a net overrides all drivers of the net, until a *release* is executed on the net

```
.....  
or #1 (PRT, STD, DXZ);  
  
initial  
begin  
    force PRT = DXZ & STD;  
    #5                // Wait for 5 time units.  
    release PRT;  
    $finish;  
end
```

High-Level Constructs

- ❑ if statement
- ❑ loop statement (*forever, repeat, while, for*)
- ❑ *case* statement

If Statement

```
if (expression)  
    statements  
{ else if (expression)  
    statements      }  
[ else  
    statements      ]
```

□ Example:

```
if (total < 60)  
begin  
    GRADE = C;  
    TOTAL_C = TOTAL_C + 1;  
end  
else if (SUM < 75)  
    GRADE = B;  
else  
    GRADE = A;
```

Case Statement

```
case (case_expression)  
    case_item_expression {, case_item_expression} : statements  
    .....  
    .....  
    [ default: statements ]  
endcase
```

- ❑ *case_expression* is evaluated first
- ❑ *case_item_expressions* are evaluated and compared in the order given
- ❑ *case_expressions* or *case_item_expressions* need not be constant expressions
- ❑ .
- ❑ x and z values are compared as well

An Example

```
wire [3:0] A, B;  
  reg [3:0] Z;  
  
  parameter ADD_INSTR = 2'b10, SUB_INSTR = 2'b11;  
             MULT_INSTR = 2'b01, DIV_INSTR = 2'b00;  
  
  case (OP_CODE),  
    ADD_INSTR:    Z = A + B;  
    SUB_INSTR:    Z = A - B;  
    MULT_INSTR:   Z = A * B;  
    DIV_INSTR:    Z = A / B;  
  endcase
```

Don't-Care in Case

- ❑ *casez* considers *z* values (in case-expression and in case_intem_expressions) as don't-cares
- ❑ *casex* statement consider *x* and *z* values as don't-cares

```
casez (MASK);  
    4'b1???:    DBUS[4] = 0;  
    4'b01??:    DBUS[3] = 0;  
    4'b001?:    DBUS[2] = 0;  
    4'b0001:    DBUS[1] = 0;  
endcase
```

- ❑ A *z* value is same as a *?* in a literal to mean a don't-care

Sequential Statements in a Block

❑ “case” statement

- » Specifies a multi-way branch based on the value of an expression.
- » Is sequential and therefore may be nested to any level.
- » \$parallel ensures not priority encoded (less logic)

```
module EX_CASE (A, B, F, D, H, N);
    input A, B;
    input [3:0] F;
    inout H, N;
    output [1:0] D;
    reg H, N;
    reg [1:0] D;
    always @(A or B or F or H or N)
    begin
        case (F) // $parallel
            0, 4, 8, 9: D = {H, A};
            5: N = N & B;
            7: H = B;
            default: begin
                D = {H, A}; N = N & A; H = B;
            end
        endcase
    end
endmodule
```

Case Statement

□ Full and Parallel

```
module FULL (c1, c2, c3, c4, a, y);
    input c1, c2, c3, c4;
    output y;
    input [1:0] a;
    output [6:0] y;
    reg [6:0] y;
    always @ (posedge Pclk)
    begin
        if (Preset)
            begin
                y <= #2 {6'b0, 1'b0};
            end
        else casex ({c1, c2, c3, c4}) // $full $parallel
            4'b1x0x:      y[0] <= #2 a[0];
            4'b1x1x:      y[1:0] <= #2 a;
            4'b01x0:      y <= #2 y + 7'b1;
            4'b0101:      y <= #2 {y[6:1]+6'b1, 1'b0};
            4'b1111:      y <= #2 {y[6:2]+5'b1, 2'b0};
        endcase
    end
end
```

Forever and Repeat

❑ *forever-loop* statement

forever

statements

// should only be used with timing controls or with the **disable** statement

forever

#10 CLOCK = ~CLOCK;

❑ *repeat-loop* statement

repeat (*loop-count*)

statements

repeat (FAC)

FACSUM = FACSUM + FAC;

repeat (shift_by)

P_reg = P_reg << 1;

While and For

□ *while-loop* statement

```
forever (condition)  
    statements  
while (BY > 0)  
begin  
    acc = acc << 1;  
    BY = BY - 1;  
end
```

□ *for-loop* statement

```
for (initial_assignment; condition; step_assignment)  
    statements  
integer K; // K must be of register type  
for (k=0; K<Max_range; K=K+1)  
begin  
    if (ABUS[K] == 0) ABUS[K] = 1;  
    else if (ABUS[K] == 1) ABUS[K] = 0;  
    else $display ("ABUS[K] is an x or an z");  
end
```

“For” - “Loop” Statement

- ❑ Nested for-loops supported
- ❑ A synchronous logic block is not allowed within a for-loop statement
- ❑ Example (“for”- “loop”)

```
for (J=5; J<8; J=J+4)
```

```
begin
```

```
    F = J + E;
```

```
    C = F;
```

```
end
```

“Repeat” - “Loop” Statement

- ❑ Nested repeat-loops supported
- ❑ A synchronous logic block is not allowed within a repeat-loop statement
- ❑ Example (“repeat”- “loop”)

```
parameter size = 5;  
repeat (size)  
begin  
    H = A = B;  
    I = H*3;  
end
```


Timing Controls

- ❑ Timing control over when procedural statements can occur
- ❑ Delay control
 - » *# delay*
 - » Timing duration from time initially encountered the statement to the time it executes
- ❑ Event control
 - » Statement execution is delayed until the occurrence of some simulation event
 - » *@ symbol*
 - » Edge-triggered control
 - » Level-sensitive control

Delay Control

- ❑ The procedural statement execution is delayed by the specified delay
- ❑ If delay expression is x or z, it is 0
- ❑ If delay expression is negative, use two's complement unsigned integer

#2 TX = RX - 5;

STROBE COMPARE = TX ^ MASK;

#(PERIOD/2) CLOCK = ~CLOCK;

Edge-Triggered Event Control

```
@ (posedge CLOCK)          CURR_STATE = NEXT_STATE;
@ (posedge RESET) COUNT = 0;
@ (CTRL_A or CTRL_B)      DBUS = 'bz;
@ CLA ZOO = FOO;
// Assign on any change of value in register CLA.
@ (posedge CLEAR or negedge RESET)      Q = 0;
```

- ❑ Negative edge: (1->x, z, or 0), (x or z -> 0)
- ❑ Positive edge: (0->x, z, or 0), (x or z -> 1)
- ❑ Events can be OR'ed as well to indicate “if any one of the events occur”

Levels-Sensitive Event Control

- ❑ Execution of a procedural statement is delayed until a condition becomes true
- ❑ wait statement:
 wait (*condition*)
 statement
- ❑ If condition is already true, the next statement is evaluated immediately.
 wait (SUM > 22) SUM = 0;

Intra-assignment Timing Control

- ❑ Timing control within an assignment
- ❑ Delay assigning right-hand side to left-hand side
- ❑ Right-hand side expression is evaluated before the delay

```
DONE = #5 A;  
// is the same as  
begin  
    temp = A;  
    #5 DONE = temp;  
end
```

```
Q = @ (posedge CLK) D;  
// is the same as  
begin  
    temp = D;  
    @ (posedge CLK) Q = temp;  
end
```

Example

- ❑ Negative edge-triggered D flip-flop with asynchronous preset:

```
module DFF (CLK, D, PRESET, Q, QBAR);
    input CLK, D, PRESET;
    output Q, QBAR;
    reg Q, QBAR;

    always wait (PRESET == 1)
    begin
        #3 Q = 1;
        #2 QBAR = 0;
        wait (PRESET == 0);
    end
    always @ (negedge CLK)
    begin
        if (PRESET != 1)
        begin
            #5 Q = D;
            #1 QBAR = ~Q;
        end
    end
endmodule
```

Block Statement

- ❑ Grouping of statements as one statement
- ❑ Two types:
 - » *Sequential* block (*begin-end* block):
Statements are executed sequentially in the given order
 - » *Parallel* block (*fork-join* block):
Statements in the block executed concurrently
- ❑ Blocks can be named optionally
 - » Registers can be declared locally
 - » Blocks can be referenced (*disable* statement)
 - » Can uniquely identify registers

Sequential Block

```
begin  
    [ : block_id { declarations } ]  
    statements  
end
```

```
// Waveform generation  
begin  
    #2 stream = 1;  
    #7 stream = 0;  
    #10 stream = 1;  
    #14 stream = 0;  
    #16 stream = 1;  
    #21 stream = 0;  
end
```


Parallel Block

- ❑ Control passes out of block after all statements finish

fork

[: *block_id* { *declarations* }]

statements

join

// Waveform generation

fork

#2 stream = 1;

#5 stream = 0;

#3 stream = 1;

#4 stream = 0;

#2 stream = 1;

#5 stream = 0;

join

Initial Statement

- ❑ Executes only once

initial

statements

- ❑ Used for initialization and waveform generation

// Initialization:

reg [7:0] RAM[0:1023];

reg RIB_REG;

initial

begin: SEQ_BLK_A

integer INX;

RIB_REG = 0;

for (INX=0; INX<SIZE;INX=INX+1)

RAM[INX] = 0;

end

Always Statement

- ❑ Executes continuously; must be used with some form of timing control.

always

statements

always

CLK = ~CLK;

// Will loop indefinitely


always

#5 CLK = ~CLK;

// Waveform on CLK of period 10

- ❑ Any number of *initial* and *always* statements may appear within a module
- ❑ *initial* and *always* statements all execute in parallel

Handshake Example

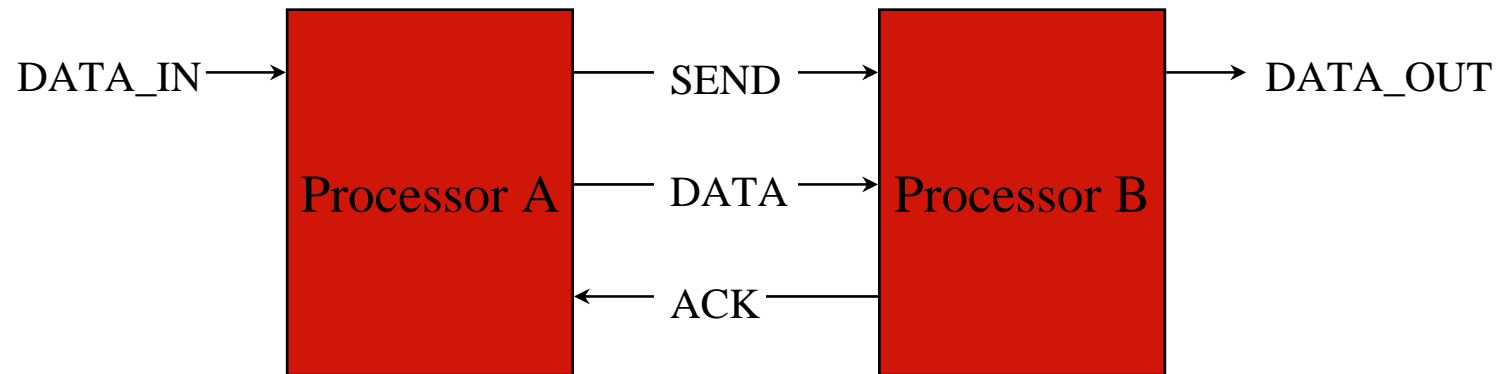

```
'timescale 1 ns/100ps
module HAND_SHAKE (DATA_IN, DATA_OUT);
    input [0:31] DATA_IN;
    output [0:31] DATA_OUT;
    reg SEND, ACK;
    reg [0:31] DATA;
    initial {ACK, SEND} = 0;
```

```
always
begin
    SEND = 1;
    DATA = DATA_IN;
    wait (ACK = 1);
    SEND = 0;
    #50;                                // Wait for 50 time units.
end

always
begin
    #25;                                // Wait for 25 time units.
    DATA_OUT = DATA;
    ACK = 1;
    #25 ACK = 0;
    wait (SEND == 1)
end
endmodule
```

Other Topics

Tasks

- ❑ Procedure
- ❑ Can contain timing control
- ❑ Can call other functions and tasks
- ❑ 0 or more arguments
- ❑ Output or input arguments can be updated
- ❑ Task definition:

```
task task_id;  
    [ declarations ]  
    statements  
endtask
```

- ❑ Cannot declare a new type within a task

Task Example

```
parameter MAXBITS = 8;

task REVERSE_BITS;
    input [MAXBITS-1 : 0] DIN;
    output [MAXBITS-1 : 0] DOUT;
    integer K;
    begin
        for (K=0;K<MAXBITS;K=K+1)
            DOUT [MAXBITS-K] = DIN[K];
        end
    endtask
```


Task Calling

- ❑ Task calling:

task_id [(*expr1*, *expr2*, . . . , *exprN*)];

- ❑ List of arguments must match the order of arguments in task definition
- ❑ Arguments are passed by value
- ❑ Task can be called more than once concurrently
- ❑ Local variables are static; if concurrently called, same local variables are shared
- ❑ Calling statement for task REVERSE_BITS:

// Declarations:

reg [MAXBITS-1 : 0] REG_X, NEW_REG_X;

REVERSE_BITS (REG_X, NEW_REG_X); // Calling task.

Tasks and Functions

- ❑ Provides the ability to call common procedures from different places within a description
- ❑ Enables large procedures to be broken into smaller ones making reading and debugging easier
- ❑ The I/O passed in a task enabling statement must match that of the I/O in the task declaration

Example: (Task)

```
task PROC
    input A, B;
    inout D;
begin
    D = A + B
end
endtask
```

Example: (Task enabling for the left task)

```
always @ (in1 or in2)
    if (in1)
        PROC (in1, Y, result);
    else if (in2)
        PROC (in2, Y, result);
```

Functions

- ❑ Executes in one simulation time unit.
- ❑ No delays.
- ❑ Cannot call another task.
- ❑ Must have at least one input.
- ❑ Returns a value that can be used in an expression.
- ❑ Function definition:

```
function [range] function_id;  
    input_declarations  
    other_declarations  
    statements  
endtask
```

- ❑ If no range is specified, 1 bit is assumed.

Function Example

```
parameter MAXBITS = 8;

function [MAXBITS-1:0] REVERSE_BITS;
    input [MAXBITS-1 : 0] DIN;
    reg K;
    begin
        for (K=0;K<MAXBITS;K=K+1)
            REVERSE_BITS [MAXBITS-K] = DIN[K];
        end
    endfunction
```

- ❑ Implicit declaration of a reg, same as function name
- ❑ Must include assignment to function name

Function Call

- ❑ Can be used in any expression

- ❑ Function call:

function_id [(*expr1*, *expr2*, . . . , *exprN*)];

- ❑ Calling function REVERSE_BITS:

// Declarations:

reg [MAXBITS-1 : 0] REG_X, NEW_REG_X;

NEW_REG_X = REVERSE_BITS (REG_X);

Function Call

- ❑ Return a value (unlike task)
- ❑ Must have at least one input argument
- ❑ May not enable task, but task may enable other tasks and functions

Example: (function)

```
function [3:0] DEPTH
    input D, T;
    reg [3:0] R, p;
    begin
        if (D)
            p = p*2;
        else if (~T)
            R = *p;
        DEPTH = R*p;
    end
endfunction
```

Example: (calling function)

```
// RESULT is a 4-bit wire
assign RESULT = DEPTH (in1, in2);
```

Hierarchy

- ❑ Module definition:

```
module module_name (port_list);  
    declarations_and_statements  
endmodule
```

- ❑ Module instantiation statement:

```
module_name instance_name (port_associations);
```

- ❑ Port associations can be positional or named; cannot be mixed

```
local_net_name                // positional  
Port_Name(local_net_name)      // Named
```

- ❑ Ports can be: input, output, inout

- ❑ Port can be declared as a net or a reg; must have same size as port

Hierarchy

- ❑ Unconnected module inputs are driven to z state
- ❑ Unconnected module outputs are simply unused

```
DFF d1 (.Q(QS), .QBAR(), .DADA(D),  
        .PRESET(), .CLOCK(CK));           // Named
```

```
DFF d2 (QS, , D, , CK);                   // Positional  
// Output QBAR is not connected  
// Input PRESET is open and hence set to value z
```


Hierarchical Instantiation

```
module sub_block1 (a, z);  
  input a;  
  output z;  
  wire a, z;  
  IV U1 (.A(a), .Z(z));  
endmodule
```

```
module sub_block2 (a, z);  
  input a;  
  output z;  
  wire a, z;  
  IV U1 (.A(a), .Z(z));  
endmodule
```

```
module top (din1, din2, dout1, dout2);  
  input din1;  
  input din2;  
  output dout1;  
  output dout2;
```


```
  wire din1, din2, dout1, dout2;
```

```
  sub_block1 U1(.a(din1), .z(dout1));  
  sub_block2 U2(.a(din2), .z(dout2));  
endmodule
```

Hierarchical Path Name

- ❑ Every identifier has a unique hierarchical path name
- ❑ Period character is the separator
- ❑ New hierarchy is defined by: module instantiation, task definition, function definition, named block

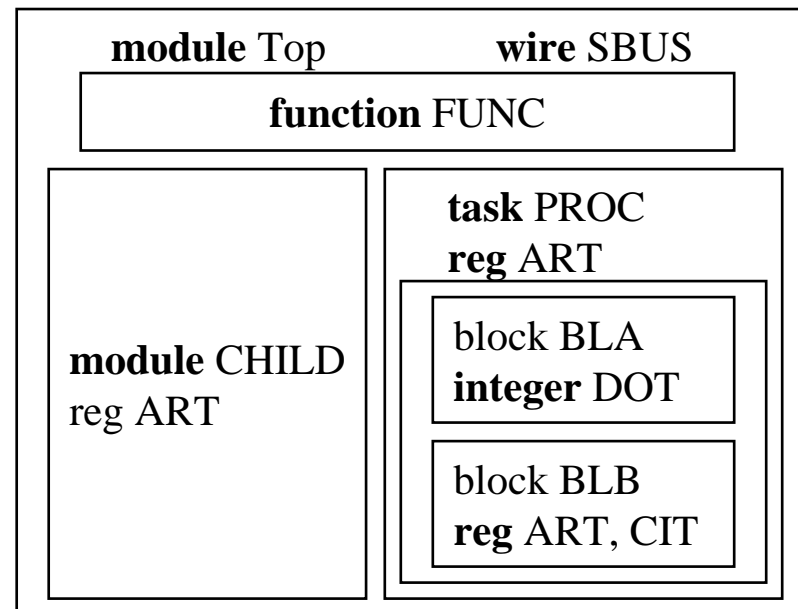TOP.CHILD.ART
TOP.PROC.ART
TOP.PROC.BLB.CIT
TOP.PROC.BLA.DOT
TOP.SBUS



Mixing Structure and Behavior

module *module_name* (*port_list*);

Declarations:

Net declarations.

Reg declarations.

Parameter declarations.

Initial statements.

Gate instantiation statements.

Module instantiation statements.

UDP instantiation statements.

Always statements.

Continuous assignment.

endmodule

Module Parameter Values

- ❑ Two ways
- ❑ Defparam statement:
 - » Parameter value in any module instance can be changed by using hierarchical name.

```
defparam FA.n1.XOR_DELAY = 2,  
          FA.n2.AND_DELAY = 3;
```

- ❑ Module instance parameter value assignment:
 - » Specify the parameter value in the module instantiation.
 - » Order of assignment is the same as order of declarations within module

```
HA # (2, 3) h1 (.A(p), .B(Q), .S(S1), .C(X1));
```

System Tasks

❑ Display System Tasks

- » **\$display** and **\$monitor** system tasks.
- » **\$write** task: Write the specified argument values to output, but does not add a newline character (as opposed to **\$display** which does)
 - \$write** | **\$writeh** | **\$writeb** | **\$writeo** (*arg1, arg2, . . . , argN*)
 - Different default bases
 - \$write** (“simulation time is ”);
 - \$write** (“%t\n”, **\$time**);
- » **\$strobe** task: Display run data at selected time but at end of current simulation time.
 - always @ (posedge RST)
 - \$strobe** (“the flip-flop value is %b at time %t”, Q, **\$time**);
 - /* After end of simulation time when RST has a positive edge, the \$strobe task prints the values of Q and current simulation time. */
- » %h, %d, %o, %b, %c, %m, %s

System Tasks (cnt'd)

❑ File I/O system tasks

- » **\$fopen**, **\$fclose**
- » **\$fdisplay**, **\$fwrite**, **\$fstrobe**, **\$fmonitor**
- » **\$readmemb**, **\$readmemh**: Loads memory data from a file

```
reg [0:3] MEM_A [0:63];  
$readmemb ("ones_and_zeros.vec", MEM_A);
```

❑ Simulation control system tasks

- » **\$finish**; // make the simulation exit
- » **\$stop**; // Causes simulation to suspend

❑ Simulation time system functions

- » **\$time** // 64-bit time value is returned
- » **\$stime** // 32-bit unsigned integer time value is returned
- » **\$realtime** // return real number time

Disable Statement

- ❑ Can be used to terminate a task or a block before it finishes executing all its statements
- ❑ Used to model hardware interrupts and global resets

disable task_id;

disable block_id;

- ❑ Execution continues with the next statement

```
begin BLK_A
```

```
    // statement 1
```

```
    disable BLK_A;
```

```
    // statement 2
```

```
end
```

```
    // statement 3
```

// Statement 2 is never executed. After disable statement is executed, statement 5 is executed

Value Change Dump File

- ❑ Contain information about value changes on specified variables in design

\$dumpfile (“uart.dump”);

\$dumpvars (level_num, CLK, CLR);

\$dumpvars; // Dumps all variables.

\$dumpoff ;

\$dumpon;

\$dumpall;

\$dumplimit (file_size);

\$dumpflush;

Compiler Directives

- ❑ Always begins with a character '**'**
- ❑ Definition holds accross multiple files for one compilation

```
'default_nettype wand           // specifies net type for implicit net
//
'define WORD 16                  // Create a macro for text substitution
'undef WORD                      // Undefines a previously defined text macro.
'ifdef SUN
...
['else
...
'endif ]                        // Conditional compilation
'include "../rx.h"              // Inserted the contents of the specified file.
'resetall                        // All compiler directives are reset to default.
'timescale 1 ns / 10 ps         // 1ns is the time unit and delays are rounded to 10ps
```

Nested Macros

```
module NESTED_MACROS (A, B, C, D, Y);  
  input A, B, C, D;  
  output Y;  
  
  reg Y;  
  
  'define ONE 1'b1  
  'define ZERO 1'b0  
  'define TEST (A == 'ONE)  
  
  always @ (A or B or C or D)  
    if ('TEST && (C != D))  
      Y = 1;  
    else  
      Y = 0;  
  
endmodule
```

Specify Block

- ❑ Used to assign delay to these paths
- ❑ Used to describe paths between a source and a destination
- ❑ Used to perform timing checks.

specify

spec_param_declarations // Declares parameters

// for use only within the specify block.

path_declarations

system_timing_checks

endspecify

Specify Block

```
specify
    specparam tCLK_Q = (4:5:6);

// Path delays:
(CLOCK*> Q) = tCLK_Q;
(DATA*> Q) = 12;
(CLEAR, PRESET*> Q) = (4:5:3);

/* Can specify pulse width to be rejected and a range for which to generate an x */

    specparam PATHPULSE$ = (1,2);
// Reject limit = 1, error limit = 2.
    specparam PATHPULSE$DATA$Q = 6;
endspecify
```

Outline

- ❑ Introduction
- ❑ Language Structure
- ❑ Modeling Part 1
- ❑ Modeling Part 2

Modeling for Synthesis

Modeling Structures

- ❑ Net-list
 - » structural description
- ❑ Primitives
- ❑ Continuous assignment
 - » Data flow specification
 - » Verilog operators
- ❑ Procedural blocks
 - » always and initial blocks
 - Allow timing control and concurrency
 - » C-like procedural statements
- ❑ Task and function

Continuous Assignments

- ❑ Model combinational logic
- ❑ Operands + operators
- ❑ Drive values to a net
 - » `assign out = a & b;`
 - » `assign eq = (a==b);`
 - » `wire #10 inv = ~in;`
 - » `wire [7:0] c = a + b;`
- ❑ Avoid logic loops
 - » `assign a = a + b;`
 - » asynchronous design

Operator Precedence

[]	bit-select or part select	>, >+, <, <=	
()	parenthesis		relational
!, ~	logic and bit-wise negation	==, !=	logical equality
&, , ~&, ~ , ^, ~^, ^~		&	bit-wise AND
	reduction operators	^, ^~, ~^	bit-wise XOR and XNOR
+, -	unary arithmetic		bit-wise OR
{ }	concatenation	&&	logical AND
*, /, %	arithmetic		logical or
+, -	arithmetic	?:	conditional
>>, <<	shift		

RTL Model

- ❑ Describe the system at a higher level of abstraction
- ❑ Specify a set of concurrently active procedural blocks
- ❑ Procedural blocks
 - » *initial* blocks
 - For test-fixtures to generate test vectors
 - » *always* blocks
 - Can be combinational circuits
 - Can infer latches or flip-flops
 - » Procedural blocks have the following components
 - Procedural assignment statements
 - timing controls
 - high-level programming language constructs

RTL Statements

- ❑ Procedural and RTL assignments
 - » reg and integer
 - » `out = a+ b;`
- ❑ begin ... end block statements
 - » group statements
- ❑ if ... else statements
- ❑ case statements
- ❑ for loops
- ❑ while loops
- ❑ forever loops
- ❑ disabled statements
 - » Disable a named block

Combinational Always Blocks

- ❑ A complete sensitivity list (inputs)

```
always @ (a or b or c)
    f = a&~c | b&c;
```

- ❑ Simulation results

```
always @ (a or b)           // conditions are ignored by synthesizer
    f = a&~c | b&c;
```

- ❑ Parentheses


```
always @ (a or b or c or d)
    z = a+b+c+d;           // z = (a+b) + (c+d);
```

Combinational Circuit Design

- ❑ Outputs are functions of inputs

- ❑ Examples

 - » Mux
- » Decoder
- » Priority encoder
- » Adder



Multiplexor

❑ Net-list (gate-level)

```
module mux2_1 (out, a, b, sel);
    output out;
    input a, b, sel;
    not (sel_, sel);
    and (a1, a, sel_);
    and (b1, b, sel);
    or (out, a1, b1);
endmodule
```

❑ Continuous assignment

```
module mux2_1 (out, a, b, sel);
    output out;
    input a, b, sel;
    assign out = (a&~sel) | (b&sel);
endmodule
```

❑ RTL modeling

```
module mux2_1 (out, a, b, sel);
    output out;
    input a, b, sel;
    always @ (a or b or sel)
        if (sel)
            out = b;
        else
            out = a;
endmodule
```

Multiplexor

❑ 4-to-1 multiplexor

```
module mux4_1 (out, in0, in1, in2, in3, sel);
    output out;
    input in0, in1, in2, in3;
    input [1:0] sel;

    assign out = (sel == 2'b00) ? in0 :
                 (sel == 2'b01) ? in1 :
                 (sel == 2'b10) ? in2 :
                 (sel == 2'b11) ? in3 :
                 1'bx;
endmodule
```

❑ 4-to-1 multiplexor

```
module mux4_1 (out, in, sel);
    output out;
    input [3:0] in;
    input [1:0] sel;
    reg out;

    always @ (sel or in) begin
        case (sel)
            2'd0: out = in[0];
            2'd1: out = in[1];
            2'd2: out = in[2];
            2'd3: out = in[3];
            default: out = 1'bx;
        endcase
    end
endmodule
```

Decoder

❑ 3-8 decoder with an enable control

```
module decoder (o, enb_, sel);
    output [7:0] o;
    input enb_;
    input [2:0] sel;
    reg [7:0] o;
    always @ (enb_ or sel)
        if (enb_)
            o = 8'b1111_1111;
        else
            case (sel)
                3'b000: o = 8'b1111_1110;
                3'b001: o = 8'b1111_1101;
                3'b010: o = 8'b1111_1011;
                3'b011: o = 8'b1111_0111;
                3'b100: o = 8'b1110_1111;
                3'b101: o = 8'b1101_1111;
                3'b110: o = 8'b1011_1111;
                3'b111: o = 8'b0111_1111;
                default: o = 8'bx;
            endcase
    endmodule
```


Priority Encoder

always @ (d0 or d1 or d2 or d3)

if (d3 == 1)

{x, y, v} = 3'b111;

else if (d2 == 1)

{x, y, v} = 3'b101;

else if (d1 == 1)

{x, y, v} = 3'b011;

else if (d0 == 1)

{x, y, v} = 3'b001;

else

{x, y, v} = 3'bxx0;

inputs				outputs		
d0	d1	d2	d3	x	y	v
0	0	0	0	x	x	0
1	0	0	0	0	0	1
x	1	0	0	0	1	1
x	x	1	0	1	0	1
x	x	x	1	1	1	1

Parity Checker

```
module parity_checker (data, parity);  
    input [0:7] data;  
    output parity;  
    reg parity;  
    always @ (data)  
    begin: check_parity  
        reg partial;  
        integer n;  
        partial = data[0];  
        for (n=1; n<=7; n=n+1)  
        begin  
            partial = partial^data[n];  
        end  
        parity <= partial;  
    end  
endmodule
```

Adder

❑ RTL modeling


```
module adder (c, s, a, b);  
    output c;  
    output [7:0] s;  
    input [7:0] a, b;
```

```
    assign {c, s} = a + b;  
endmodule
```

❑ Logic synthesis

- » Carry Look-Ahead (CLA) adder for speed optimization
- » Ripple adder for area optimization

Sequential Circuit Design

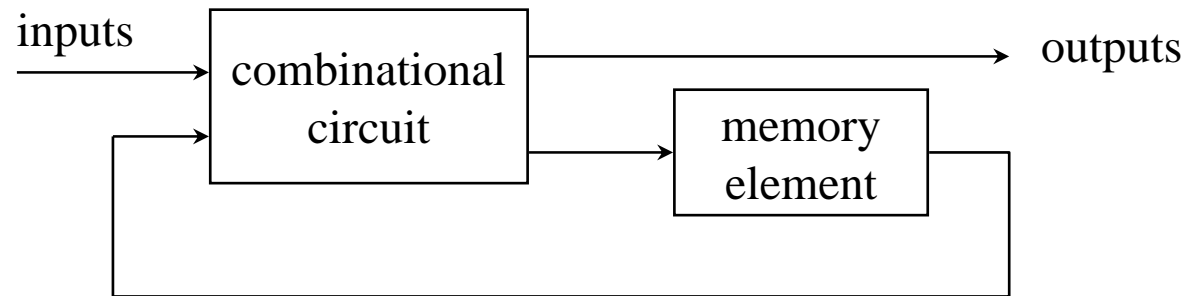

- ❑ A feedback path
- ❑ The state of the sequential circuits
- ❑ The state transition
 - » Synchronous circuits
 - » Asynchronous circuits

Register Inference

❑ Inference of Positive Edge Triggered Flip-flops

```
module ff1 (data, clk, q);  
    input [3:0] data;  
    input clk;  
    output [3:0] q;  
    reg [3:0] q;  
    always (posedge clk)  
        q = data;  
endmodule
```


❑ Inference of Positive Edge Triggered Flip-flops with active low reset

```
module inf_ff (clk, reset, a, b, q);  
    input clk, reset;  
    input [3:0] a, b;  
    output [3:0] q;  
    reg [3:0] q;  
    always (posedge clk or negedge reset)  
        if (!reset) q = 0;           // asynchronous input first  
        else q = a&b;  
endmodule
```

Variable Within Always

- ❑ Redundant register variables can cause extra logics

 
```
module BAD_DESIGN (D, CLK, RN, Q, QBAR);  
    input D, CLK, RN;  
    output Q, QBAR;  
    reg Q, QBAR;  
  
    always (negedge RN or posedge CLK)  
    begin  
        if (! RN) begin  
            Q = 1'b0;  
            QBAR = 1'b1;  
        end  
        else begin  
            Q = D;  
            QBAR = ~D;  
        end  
    end  
  
endmodule
```



Variable Within Always

```
module GOOD_DESIGN (D, CLK, RN, Q, QBAR);
  input D, CLK, RN;
  output Q, QBAR;
  reg Q, QBAR;

   always (negedge RN or posedge CLK)
  begin
    if (! RN)
      Q = 1'b0;
    else
      Q = D;
    end
    assign QBAR = ~Q;
  endmodule
```



D Latches

❑ D latch

always @ (enable or data)

if (enable)


q = data;

❑ D latch with gated asynchronous data

always @ (enable or data or gate)

if (enable)

q = data&gate;

 

Latches

❑ D latch with gated “enable”

always @ (enable or data or gate)

if (enable&gate)

q = data;

❑ D latch with asynchronous reset


always @ (reset or data)

if (reset)

q = 1'b0;

else if (enable)

q = data;

 

Latch Inference

□ What if g is false?

```
module latch4 (d, en, g, k);  
    input [3:0] d;  
    input en, g;  
    output [3:0] k;  
    reg [3:0] k;  
    always (d or en or g)  
        if (g)  
            k = d & {en, en, en, en};  
endmodule
```

□ y and z are not fully specified

```
always @ (control or a or b or c) begin  
    if (control > 2)  
        begin  
            x = a;  
            y = b;  
            z = c;  
        end  
    else x = b;  
end
```

Latch Inference

- ❑ What if bcd is 5?

```
wire [3:0] bcd;  
...  
case (bcd)  
  4'd0: begin zero = 1'b1; {one, two} = 2'b0; end  
  4'd1: begin {zero, two} = 2'b0; one = 1'b1; end  
  4'd2: begin {zero, one} = 2'b0; two = 1'b1; end  
Endcase
```

- ❑ Using default to prevent latch inference

```
wire [3:0] bcd;  
...  
case (bcd)  
  4'd0: begin zero = 1'b1; {one, two} = 2'b0; end  
  4'd1: begin {zero, two} = 2'b0; one = 1'b1; end  
  4'd1: begin {zero, one} = 2'b0; two = 1'b1; end  
  default: {zero, one, two} = 3'bxxx;  
endcase
```

Latch Inference

- Why latches are inferred?


```
wire [3:0] bcd;  
...  
case (bcd)  
  4'd0: zero = 1'b1;  
  4'd1: one = 1'b1;  
  4'd1: two = 1'b1;  
  default: {zero, one, two} = 3'xxx;  
endcase
```

- Using full_case directive to prevent latch inference

```
wire [3:0] bcd;  
...  
case (bcd) //synopsys full_case  
  4'd0: begin zero = 1'b1; {one, two} = 2'b0; end  
  4'd1: begin {zero, two} = 2'b0; one = 1'b1; end  
  4'd1: begin {zero, one} = 2'b0; two = 1'b1; end  
endcase
```

Registered Three-State
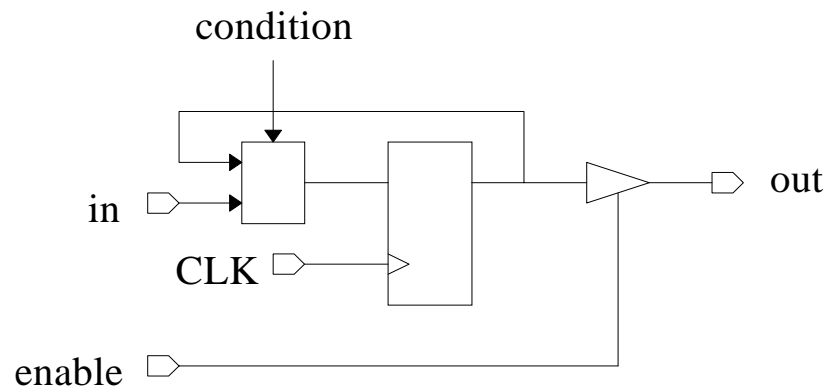
```
always (posedge CLK)
begin
    if (enable)
        out = (~condition) ? in : out;
    else
        out = 1'bz;
end
```



Inefficient Description

```
module count ( clock, reset, and_bits, or_bits, xor_bits);  
input clock, reset;  
output and_bits, or_bits, xor_bits;  
reg and_bits, or_bits, xor_bits;  
reg [2:0] count;  
always @ (posedge clock) begin  
    if (reset)  
        count = 0;  
    else  
        begin  
            count = count + 1;  
            and_bits = &count;  
            or_bits = |count;  
            xor_bits = ^count;  
        end  
    end  
end  
Endmodule
```

- ❑ Six inferred registers


Efficient Description

- ❑ Separate combinational and sequential circuits


```
module count ( clock, reset, and_bits, or_bits, xor_bits);  
  input clock, reset;  
  output and_bits, or_bits, xor_bits;  
  reg and_bits, or_bits, xor_bits;  
  reg [2:0] count;  
  always @ (posedge clock) begin  
    if (reset)  
      count = 0;  
    else  
      count = count + 1;  
  end  
  always @ (count) begin          // combinational circuits  
    and_bits = &count;  
    or_bits = |count;  
    xor_bits = ^count;  
  end  
endmodule
```

- ❑ Three registers are inferred

Pipelines

 


□ An example

 


```
assign n_sum = a + b;  
assign p = sum*d_c;  
// plus D flip-flops
```


Finite State Machine

□ Moore model

 

□ Mealy model

 


Mealy Machine Example

```
module mealy (in1, in2, clk, reset, out);
input in1, in2, clk, reset;
output out;
reg present_state, next_state, out;
// state flip-flops
always @ (posedge clk or negedge reset)
    if (!reset)
        present_state = 0;
    else
        present_state = next_state;
// combinational circuits
always @ (in1 or in2 or present_state)
    case (present_state)
        0: begin
            next_state = 1;
            out = 1'b0;
        end
        1: begin
            next_state = 0;
            out = 1'b1;
        end
    endcase
endmodule
```

A FSM Example

❑ Traffic Light Controller

 

Specification

❑ Input Signal

Reset

Description

place control in initial state

C

detects vehicle on farmroad in either direction

TS

short timer interval has expired

TL

long timer interval has expired

❑ Output Signal

HG, HY, HR

Description

assert green, yellow, red highway lights

FG, FY, FR

assert green, yellow, red farmroad lights

ST

commence timing a long or short interval

❑ State

S0

Description

highway green (farmroad red)

S1

highway yellow (farmroad red)


S2

farmroad green (highway red)

S3

farmroad yellow (highway red)

State Transition Diagram

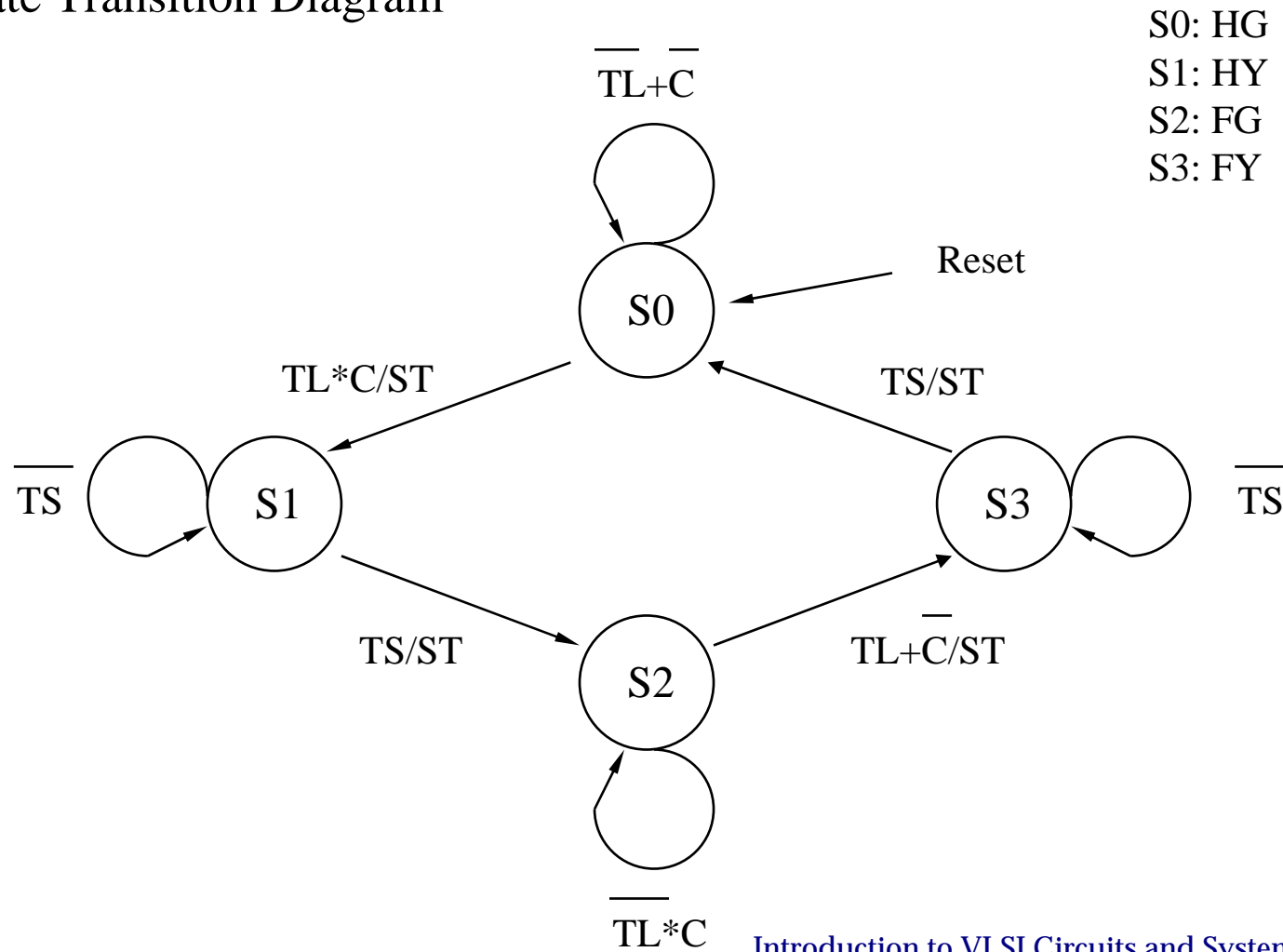

Verilog Description


```
module traffic_light (HG, HY, HR, FG, FY, FR, ST_o, tl, ts, clk, reset, c);
output HG, HY, HR, FG, FY, FR, ST_o;
input tl, ts, clk, reset, c;
reg ST_o, ST;
reg [0:1] state, next_state;
parameter EVEN=0, ODD=1;
parameter S0=2b'00, S1=2b'01, S2=2b'10, S3=2b'11;
assign HG = (state==S0);
assign HY = (state==S1);
assign HR = (state==S2) || (state==S3);
assign FG = (state==S2);
assign FY = (state==S3);
assign FR = (state==S0) || (state==S1);
```

```
//flip-flops
always @(posedge clk or posedge reset)
  if (reset) // an asynchronous reset
    begin
      state = S0;
      ST_o = 0;
    end
  else
    begin
      state = next_state;
      ST_o = ST;
    end
  end
```

```

always @(state or c or tl or ts)
  case (state)          // state transition
  S0:
    if (tl & c)
    begin
      next_state = S1;
      ST = 1;
    end
    else
    begin
      next_state = S0;
      ST = 0;
    end
  end


```

 


```

S1:
  if (ts) begin
    next_state = S2;
    ST = 1;
  end
  else begin
    next_state = S1;
    ST = 0;
  end
S2:
  if (tl | !c) begin
    next_state = S3;
    ST = 1;
  end
  else begin
    next_state = S2;
    ST = 0;
  end


```

 

```

S3:
  if (ts)
    begin
      next_state = S0;
      ST = 1;
    end
  else
    begin
      next_state = S3;
      ST = 0;
    end
  endcase
endmodule

```

 

FSM 1

```
module FSM1(CLK, OP1, OP2);
  input CLK;
  output OP1, OP2;
  reg OP1, OP2;
  parameter S0=0, S1=1, S2=2;
  reg [1:0] STATE;
  always @(posedge CLK)
  begin
    case (STATE)
      S0: begin
        OP1 = 1;
        OP2 = 1;
        STATE=S1;
      end
    end
```

```
      S1: begin
        OP1 = 0;
        STATE=S2;
      end
      S2: begin
        OP2 = 0;
        STATE=S0;
      end
      default:
        STATE=S0;
    endcase
  end
endmodule
```

FSM 2

```
module FSM2(CONTROL, CLK, RESET, Y);
  input control, CLK, RESET;
  output [0:2] Y;
  reg [0:2] Y;
  parameter S0=0, S1=1, S2=2, S3=3;
  reg [1:0] STATE;
  always @(posedge CLK)
  begin
    if (RESET) begin
      Y=0;
      STATE=S0;
    end
    else
      case (STATE)
        S0: begin
          Y = 1;
          STATE=S1;
        end

```

```
        S1: begin
          Y = 2;
          if (CONTROL == 1)
            STATE=S2;
          else
            STATE=S3;
        end
        S2: begin
          Y=3;
          STATE=S3;
        end
        S3: begin
          Y=4;
          STATE=S0;
        end
        default:
          STATE=S0;
      endcase
    end
  endmodule
```

FSM 3

```
module FSM3(CONTROL, CLK, RESET, Y);
  input control, CLK, RESET;
  output [0:2] Y;
  reg [0:2] Y;
  parameter S0=0, S1=1, S2=2, S3=3;
  reg [1:0] STATE;
  always @(posedge RESET or posedge CLK)
  begin
    if (RESET)
      STATE=S0;
    else
      case (STATE)
        S0: STATE=S1;
        S1: if (CONTROL == 1)
          STATE=S2;
        else
          STATE=S3;
```

```
        S2: STATE=S3;
        S3: STATE=S0;
        default: STATE=S0;
      endcase
    end
  always @(STATE)
    case (STATE)
      S0: Y=1;
      S1: Y=2;
      S2: Y=3;
      S3: Y=4;
      default: Y=0;
    endcase
  end
endmodule
```

FSM 4

```
module FSM4(CONTROL, CLK, RESET, Y);
  input control, CLK, RESET;
  output [0:2] Y;
  reg [0:2] Y;
  parameter S0=0, S1=1, S2=2, S3=3;
  reg [1:0] PRESENT_STATE, NEXT_STATE;
  always @(PRESENT_STATE or CONTROL)
  begin
    Y=0;
    NEXT_STATE=S0;
    case (PRESENT_STATE)
      S0: begin
        Y=1;
        NEXT_STATE=S1;
      end
      S1: begin
        if (CONTROL == 1)
          NEXT_STATE=S2;
        else
          NEXT_STATE=S3;
```

```
      S2: begin
        Y=3;
        NEXT_STATE=S3;
      end
      S3: begin
        Y=4;
        STATE=S0;
      endcase
    end
  always @(posedge RESET or posedge
    CLK)
  begin
    if (RESET)
      PRESENT_STATE=S0;
    else
      PRESENT_STATE =
        NEXT_STATE;
    end
  endmodule
```

Z Handling

- ❑ To compare with “z” (High Impedance) use only equality operators
- ❑ Using “==” z is always evaluated FALSE
- ❑ Using “!=” z is always evaluated TRUE

Example: (z handling using “==” operator)

```
if (A == 'bz)
    B = 0;
else
    B = 1;
// B is always 1 (comparison evaluated FALSE)
```

Example: (z handling using “!=” operator)

```
if (A != 4'hz)
    B = 4'h0;
else
    B = 4'h1;
// B is always 0 in 4-bit hex (comparison evaluated TRUE)
```

Z Handling

□ Tri-state inference

- » Tri-state buffer may be inferred from the high impedance value z.
- » When the high impedance value z is assigned to a variable, the output of the tri-state buffer is disabled.

Example: (Tri-state inference using z handling)

```
module tri_state(a, b);  
    parameter N = 15;  
    input [N:0] a;  
    input enable;  
    output [N:0] b;  
  
    assign b = (enable) ? a : 16'bz;  
endmodule;
```


X Handling

X (unknown) handling

- ❑ Similar to value “z”
- ❑ Using “==” x is always evaluated FALSE
- ❑ Using “!=” x is always evaluated TRUE

Example: (x handling using “==” operator)

```
if (A == 'bx)
    B = 0;
else
    B = 1;
// B is always 1 (comparison evaluated FALSE)
```

Example: (x handling using “!=” operator)

```
if (A != 4'hx)
    B = 4'h0;
else
    B = 4'h1;
// B is always 0 in 4-bit hex (comparison evaluated TRUE)
```

Wired-AND

- ❑ Resolves the shorting of an output wire receiving multiple assignments to an AND gate
 - » Declaring “wand”

- ❑ Example

```
module mywand (a, b, c);  
    input a, b;  
    output c;  
  
    wand c;  
  
    assign c = a;  
    assign c = b;  
endmodule;
```

Wired-OR

- ❑ Resolves the shorting of an output wire receiving multiple assignments to an OR gate

- » Declaring “wor”

- ❑ Example

```
module mywor (a, b, c);  
    input a, b;  
    output c;  
  
    wor c;  
  
    assign c = a;  
    assign c = b;  
endmodule;
```

Tri-State

- ❑ Shorting of an output wire receiving multiple assignments

- » Declaring “tri”

- ❑ Example

```
module mytri (a, b, c);  
    input a, b, control;  
    output c;  
  
    tri c;  
  
    assign c = (control ? a : 'bz);  
    assign c = (control ? 'bz : b);  
endmodule;
```

Resolution Functions

□ Example

```
module T (A, B, C, D, E, Z);  
    input A, B, C, D, E;  
    output Z;  
  
    // wor BAT;  
    // wand BAT;  
    // tri BAT;  
    wire BAT;  
  
    assign BAT = A & B;  
    assign BAT = C | D;  
    assign Z = BAT | E;  
endmodule;
```

Resolution Functions

- ❑ Case 1: If BAT is a wire
 - » Warning: Unable to determine wired-logic type for multiple-driver net 'BAT'
 - » Information: Assuming multiple-driver net 'BAT' is a wired-AND
 - » Connects the drivers of BAT using an AND gate
- ❑ Case 2: If BAT is a tri
 - » Warning: In design 'T', there is 1 three-state bus with non-three state drivers.
 - » Connects the drivers of BAT using an AND gate
- ❑ Case 3: If BAT is a wand
 - » Information: In design 'T', there is 1 wired-AND net
 - » Connects the drivers of BAT using an AND gate
- ❑ Case 4: If BAT is a wor
 - » Information: In design 'T', there is 1 wired-OR net
 - » Connects the drivers of BAT using an OR gate

Resolution Functions

□ Example

```
module T (A, B, C, D, E, F, G, Z);  
  input A, B, C, D, E, F, G;  
  output Z;  
  
  // wor BAT;  
  // wand BAT;  
  tri BAT;  
  // wire BAT;  
  
  assign BAT = (F ? A&B : 'bz);  
  assign BAT = (G ? C | D : 'bz);  
  assign Z = BAT | E;  
endmodule;
```

Resolution Functions

- ❑ Case 5: If BAT is a tri
 - » BAT is shorted after tri-state gates
- ❑ Case 6: If BAT is a wire/wand/wor
 - » BAT is shorted after tri-state gates

Resolution Functions

□ Example

```
module T (A, B, C, D, E, F, G, Z);  
  input A, B, C, D, E, F, G;  
  output Z;  
  // wor BAT;  
  wand BAT;  
  // tri BAT;  
  // wire BAT;  
  
  assign BAT = (F ? A&B : 'bz);  
  assign BAT = C | D;  
  assign Z = BAT | E;  
endmodule;
```

□ Case 7: BAT is a wand/wor/tri/wire

- » Warning: In design 'T', there is 1 three-state but with non three-state drivers
- » BAT drivers are shorted

Resolution Functions

□ Example

```
module T (A, B, C, D, E, F, G, H, J, Z);  
  input A, B, C, D, E, F, G, H, J;  
  output Z;  
  wor BAT;  
  // wand BAT;  
  // tri BAT;  
  // wire BAT;  
  
  assign BAT = (F ? A&B : 'bz);  
  assign BAT = C | D;  
  assign BAT = H ^ J;  
  assign Z = BAT | E;  
endmodule;
```


□ Case 8: BAT is a wand/wor/tri/wire

- » 2nd and 3rd drivers are AND'ed. Could be a bug

If-Else Statement

```
if (A[0] == 0 && A[1] == 0)
    B = C;
else if (A[0] == 1 && A[1] == 0)
    B = D;
else if (A[0] == 0 && A[1] == 1)
    B = E;
else
    B = F;
```


If-Else Hardware Implementation

 

Case Statement

```
case (A)
  2'b00: B = C;
  2'b01: B = D;
  2'b10: B = E;
  2'b11: B = F;
endcase
```

Case Hardware Implementation

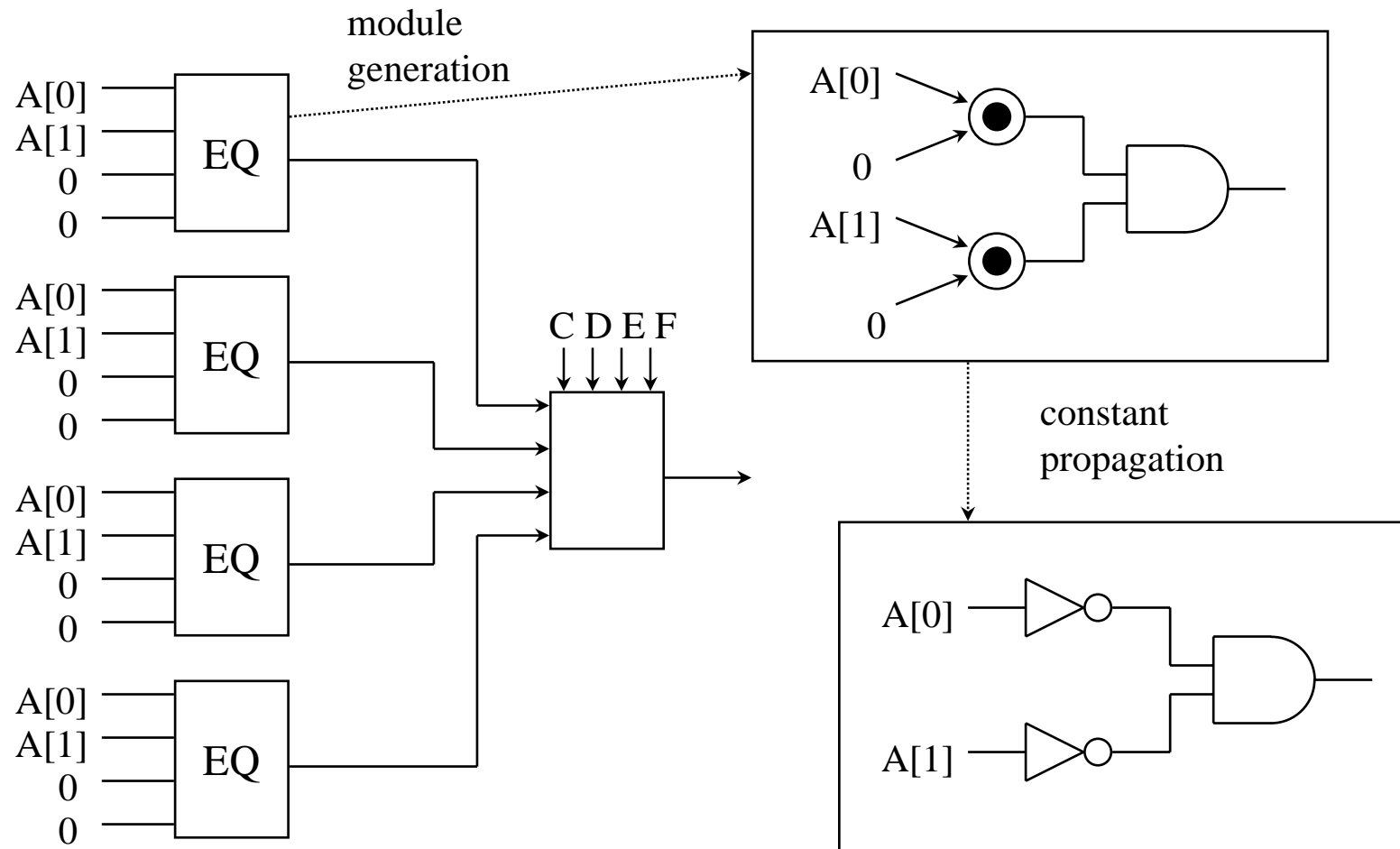

Modeling for Optimization

- ❑ Sharing common subexpressions
 - » Data path
 - » Common block of logic
 - » Sharing between synchronous and combinational sections
- ❑ Adding Structure
 - » Sharing resource explicitly
 - » Using parentheses
 - » Detailing the logic structure
- ❑ Using design knowledge
 - » Bit-width calculation
 - » Constant propagation
- ❑ Understanding hardware implication
 - » Hardware implication over software efficiency

Common Subexpression

- ❑ Don't repeatedly calculate the same operation
 - » Use temporary assignment

- ❑ Original

$$A = B + C + D;$$

$$D = F + C + B;$$

- ❑ Modified


$$E = B + C;$$

$$A = E + D;$$


$$D = F + E;$$

Using Parenthesis

$$A = B + C + D + F;$$

 

$$A = (B + C) + (D + F);$$

 

Constant Propagation

❑ Original style

```
if (RST == 'b0) begin
    A = 11 - 2;
    B = A + 1
    D = 12 - B;
    C = 2 * D;
end
else
    C = B;
```


❑ Better style

```
if (RST == 'b0)
    C = 4;
else
    C = 10;
```

Control of Logic Network

- ❑ The most straightforward coding is not always the best choice for actual hardware implementation

```
/* Verilog Version */  
module worst_ver (a, s);  
    input [4:0] a;  
    output [4:0] s;  
    reg [4:0] s; integer 1;  
    always @ (a) begin  
        if (a == 0) s = 5'b11110;  
        else begin  
            s[0] = a[0] && a[1];  
            for (I=1; I <= 4; I=I+1)  
                if (I > a-1'b1)  
                    s[I] = 1'b1;  
                else  
                    s[I] = 1'b0;  
        end  
    end  
end  
endmodule
```

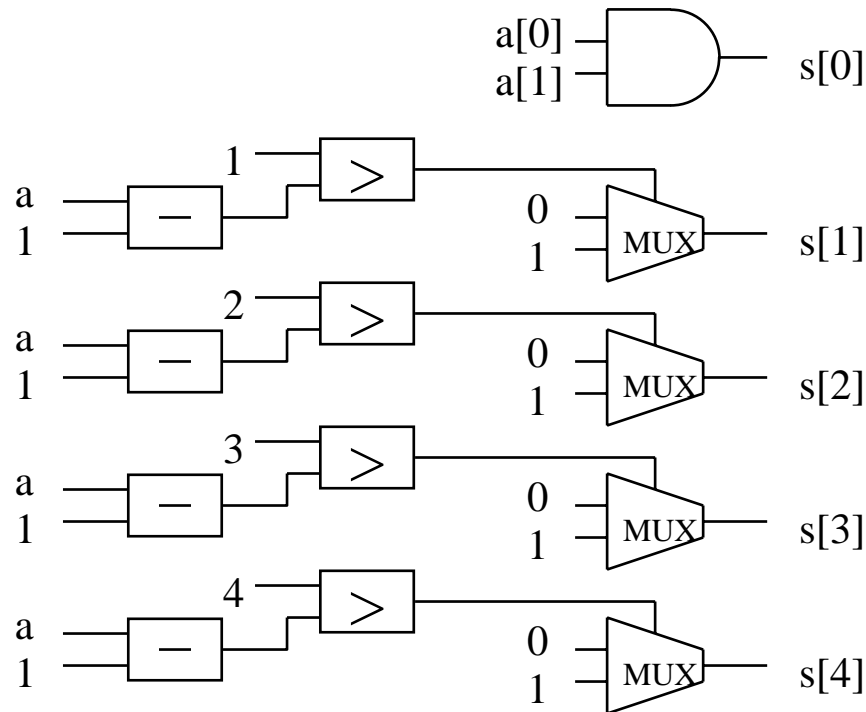


Generic logic schematic

Control of Logic Network

- Adding structure information by introduction of temporary variables

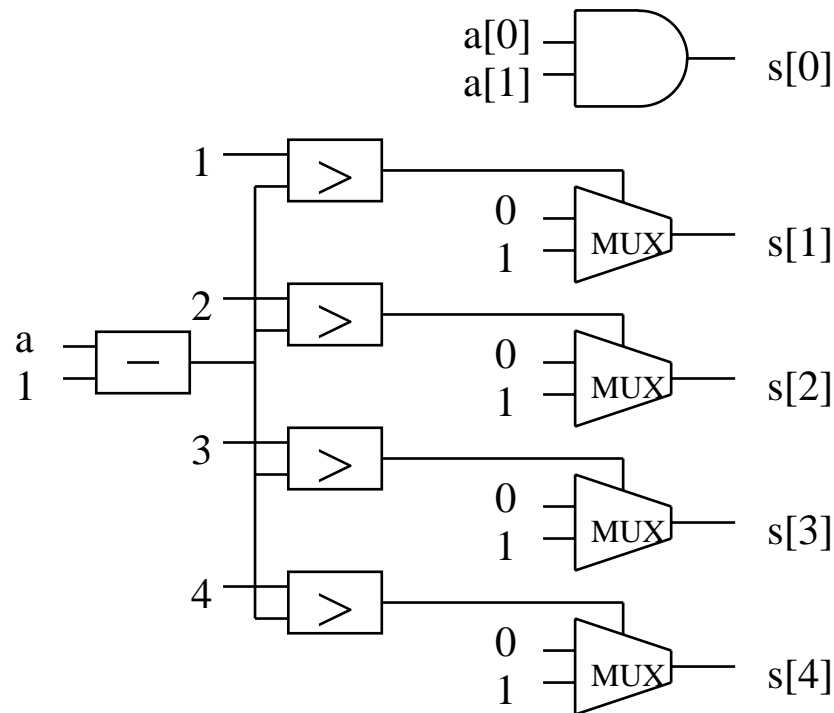
```
/* Verilog Version */  
module worse_ver (a, s);  
  input [4:0] a;  
  output [4:0] s;  
  reg [4:0] s, tmp;  
  integer 1;  
  always @ (a) begin  
    if (a == 0) s = 5'b11110;  
    else begin  
      s[0] = a[0] && a[1];  
      tmp = a-1;  
      for (I=1; I <= 4; I=I+1)  
        if (I > tmp) s[I] = 1'b1;  
        else s[I] = 1'b0;  
    end  
  end  
endmodule
```



Control of Logic Network

□ Move constants to one side

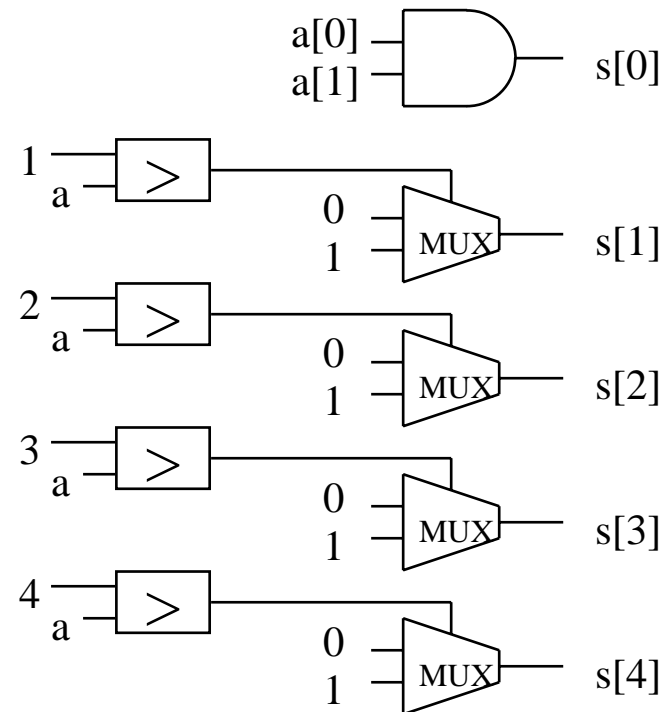
```
/* Verilog Version */
module good_ver (a, s);
  input [4:0] a;
  output [4:0] s;
  reg [4:0] s;
  integer 1;
  always @ (a) begin
    if (a == 0) s = 5'b11110;
    else begin
      s[0] = a[0] && a[1];
      for (I=1; I <= 4; I=I+1)
        if (I+1 > a)
          s[I] = 1'b1;
        else
          s[I] = 1'b0;
    end
  end
endmodule
```



Control of Logic Network

- ❑ Think more as a logic specification than a function specification

```
/* Verilog Version */  
module better_ver (a, s);  
    input [4:0] a;  
    output [4:0] s;  
    reg [4:0] s;  
    integer 1;  
    always @ (a) begin  
        case (a)  
            5'b00000: s = 5'b11110;  
            5'b00001: s = 5'b11110;  
            5'b00010: s = 5'b11100;  
            5'b00011: s = 5'b11001;  
            5'b00100: s = 5'b10000;  
            default: s={4'b0000,a[0]&& a[1]};  
        endcase  
    end  
endmodule
```

 

Generic logic schematic

Hardware Implication

- ❑ Smart comparison

- if (CTRL >= 3'b100)
 - if (CTRL[2] == 1'b1)

- ❑ Multiplication vs. shifting

- A * 4
 - A << 2

- ❑ Unnecessary operation

- if ((cnt+1) == 120)
 - if (cnt == 119)

Complex Operation

- ❑ Multiplication, division and remainder by variables or constants (not power of 2)
- ❑ Addition and subtraction by variables
- ❑ Shifting by non-computable amount
- ❑ Non-computable array indexing
- ❑ Comparison with variables
- ❑ Preferred actions:
 - » Avoiding
 - » Simplifying
 - » Sharing