



國立勤益科技大學


National Chin-Yi University of Technology

Introduction to VLSI Circuits and Systems

積體電路概論

Chapter 09

 Advanced Techniques in CMOS Logic Circuits



賴秉樑

Dept. of Electronic Engineering

National Chin-Yi University of Technology


Fall 2007

Outline

- ❑ Mirror Circuits
- ❑ Pseudo-nMOS
- ❑ Tri-State Circuits
- ❑ Clocked CMOS
- ❑ Dynamic CMOS Logic Circuits
- ❑ Dual-Rail Logic Networks


Mirror Circuits

 - ❑ Mirror circuits are based on series-parallel logic gates, but are usually faster and have a more uniform layout
 - » Output 0's imply that an nFET chain is conducting to ground
 - » Output 1's means that a pFET group provides support from the power supply




a	b	$a \oplus b$	On devices
0	0	0	← nFET
0	1	1	← pFET
1	0	1	← pFET
1	1	0	← nFET

Figure 9.1 XOR function table

 

(a) Circuit

 

(b) Layout

Figure 9.2 XOR mirror circuit

XOR & XNOR

- The advantages of the mirror circuit are more *symmetric layouts* and *shorter rise and fall times*
- In Figure 9.3, transient calculations of XOR

$$\tau_x = C_{out}(2R_x) + C_x R_x \quad (9.1)$$

where x is p or n

$$t_r \approx 2.2\tau_p \quad (9.2)$$

$$t_f \approx 2.2\tau_n \quad (9.3)$$

- In Figure 9.4, an example of XNOR

$$\overline{a \oplus b} = \overline{a \cdot b + a \cdot \bar{b}} \quad (9.4)$$

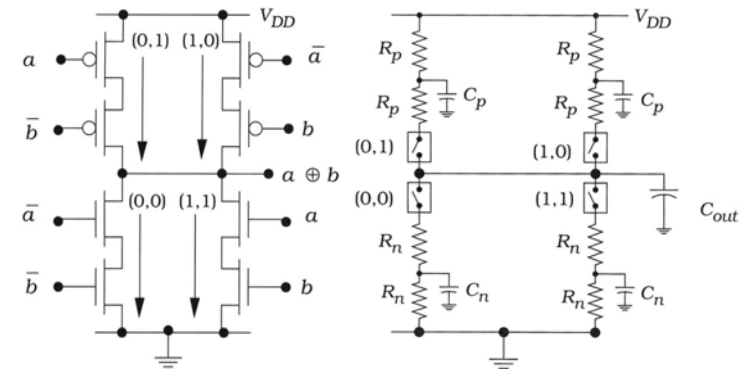


Figure 9.3 Switching mode for transient calculations (XOR)

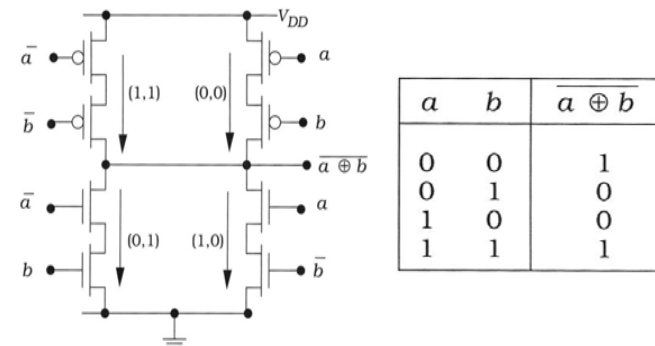


Figure 9.4 Exclusive-NOR (XNOR) circuit

Outline

- ❑ Mirror Circuits
- ❑ Pseudo-nMOS
- ❑ Tri-State Circuits
- ❑ Clocked CMOS
- ❑ Dynamic CMOS Logic Circuits
- ❑ Dual-Rail Logic Networks

Pseudo-nMOS

- ❑ Adding a single pFET to otherwise nFET-only circuit produces a logic family that is called pseudo-nMOS
 - » Less transistor than CMOS
 - » For N inputs, only requires $(N+1)$ FETs
 - » **Pull-up device**: pFET is biased active since the grounded gate gives $V_{SGp} = V_{DD}$
 - » **Pull-down device**: nFET logic array acts as a large switch between the output f and ground
 - » However, since the pFET is always biased on, V_{OL} can never achieve the ideal value of 0 V
- ❑ A simple inverter using pseudo-nMOS as Figure 9.6

$$\frac{\beta_n}{2} [2(V_{DD} - V_{Tn})V_{OL} - V_{OL}^2] = \frac{\beta_p}{2} (V_{DD} - |V_{Tp}|)^2 \quad (9.4)$$

$$V_{OL} = (V_{DD} - V_{Tn}) - \sqrt{(V_{DD} - V_{Tn})^2 - \frac{\beta_p}{\beta_n} (V_{DD} - |V_{Tp}|)^2} \quad (9.5)$$

 


Figure 9.5 General structure of a pseudo-nMOS logic gate


 



Figure 9.6 Pseudo-nMOS inverter

nFET Array in Pseudo-nMOS

 - ❑ The design of nFET array of pseudo-nMOS is the same as in standard CMOS
 - » Series and parallel logic FETs
 - » Smaller simpler layouts, and interconnect is much simpler
 - » However, the sizes need to be adjusted to insure proper electrical coupling to the next stage
 - » Resize in physical design




(a) NOR2

 


(b) NAND2

Figure 9.7 Pseudo-nMOS NOR and NAND gates

 

(a) General circuit

 

(b) Layout


Figure 9.8 AOI gate

Outline

- ❑ Mirror Circuits
- ❑ Pseudo-nMOS
- ❑ Tri-State Circuits
- ❑ Clocked CMOS
- ❑ Dynamic CMOS Logic Circuits
- ❑ Dual-Rail Logic Networks


Tri-State Circuits

 - ❑ A tri-state circuit produces the usual 0 and 1 voltages, but also has a third high impedance Z (or Hi-Z)
 - » Useful for isolating circuits from common bus lines
 - » In Hi-Z case, the output capacitance can hold a voltage even though a hardware connection exists
- ❑ A non-inverting circuit (a buffer) can be obtained by adding a regular static inverter to the input



En	f
0	Z
1	\overline{Data}

(a) Symbol and operation

 

(b) CMOS circuit

 


Figure 9.10 Tri-state layout

Figure 9.9 Tri-state inverter

Outline

- ❑ Mirror Circuits
- ❑ Pseudo-nMOS
- ❑ Tri-State Circuits
- ❑ Clocked CMOS
- ❑ Dynamic CMOS Logic Circuits
- ❑ Dual-Rail Logic Networks

Clock-CMOS (C²MOS)

- ❑ *Static CMOS*: the output of a static logic gate is valid so long as the input value are valid and the circuit has stabilized
- ❑ However, logic delays are due to the “rippling” through the circuits
 - » Not reference to any specific time base
 - » So on, Clock CMOS, or C²MOS is proposed
- ❑ C²MOS concept: non-overlapping clock

$$\phi(t) \cdot \bar{\phi}(t) = 0 \quad (9.9)$$

$$\Rightarrow \bar{\phi}(t) = V_{DD} - \phi(t) \quad (9.10)$$

- » But in physical signal, the clocks may overlap slightly during a transition

 


Figure 9.11 Clock signals

C²MOS Networks

- ❑ C2MOS is composed of a static logic circuit with tri-state output network (made up of FETs M1 and M2) that is controlled by ϕ and $\bar{\phi}$
 - » When $\phi = 0$, both M1 and M2 are active, and become to a standard static logic gate
 - » When $\phi = 1$, both M1 and M2 are cutoff, so the output is a Hi-Z state



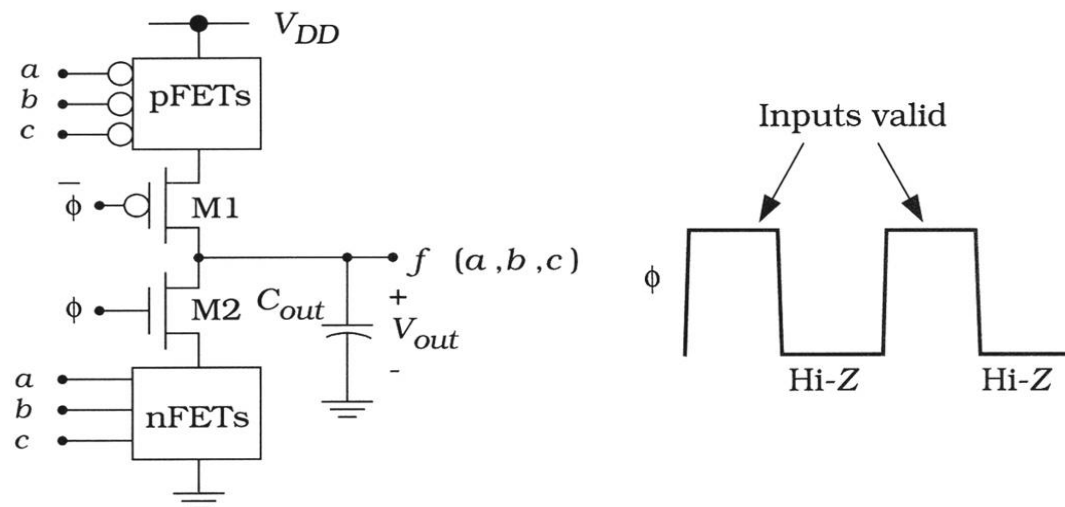


Figure 9.12 Structure of a C²MOS gate

Example of C²MOS

 


(a) NAND2

 


(b) NOR2

Figure 9.13 Example of C²MOS logic gate

 

(a) Inverter

 

(b) NAND2

Figure 9.14 Layout examples of C²MOS circuits

Leakage in C²MOS (1/2)

- ❑ *Charge leakage*: since the output node cannot hold the charge on V_{out} very long
 - » This places a lower limit on the allowable clock frequency
- ❑ If a voltage is applied to the drain or source, a small leakage current flows into, or out of, the device
 - » One reason is due to the required bulk connections
 - » The current off of the capacitor by i_{out}


$$i_{out} = i_n - i_p \quad (9.11)$$

$$= -C_{out} \frac{dV}{dt}$$


$$I_L = -C_{out} \frac{dV}{dt} \quad (9.12)$$

$$\int_{V_1}^{V(t)} dV = -\int_0^t \left(\frac{I_L}{C_{out}} \right) dt \quad (9.13)$$
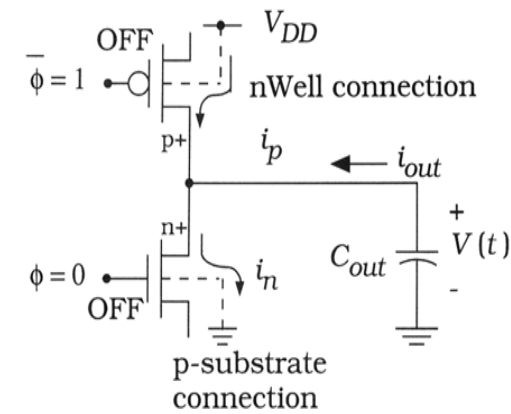
$$V(t) = V_1 - \left(\frac{I_L}{C_{out}} \right) t \quad (9.14)$$



(a) Bulk leakage currents

 

(b) Logic 1 voltage decay

Figure 9.15 Charge leakage problem

Leakage in C²MOS (2/2)

$$V(t_h) = V_1 - \left(\frac{I_L}{C_{out}} \right) t_h = V_x \quad (9.15)$$

$$t_h = \left(\frac{C_{out}}{I_L} \right) (V_1 - V_x) \quad (9.16)$$

$$t_h = \left(\frac{50 \times 10^{-15}}{10^{-13}} \right) (1) = 0.5 \text{ sec} \quad (9.17)$$

$$V(t) = \left(\frac{I_L}{C_{out}} \right) t \quad (9.18)$$


$$I = I_{D0} \left(\frac{W}{L} \right) e^{-(V_{GS} - V_T)/(nV_{th})} \quad (9.19)$$

$$t_h = \left(\frac{50 \times 15^{-15}}{10^{-9}} \right) (1) = 50 \text{ } \mu\text{sec} \quad (9.20)$$


$$t_h = \left(\frac{50 \times 15^{-15}}{10^{-7}} \right) (1) = 0.5 \text{ } \mu\text{sec} \quad (9.21)$$

$$I_L(V) = -C_{out}(V) \frac{dV}{dt} \quad (9.22)$$
 
$$\int_0^t dt = \int_{V_x}^{V(t)} \frac{C_{out}(V)}{I_L(V)} dV = t \quad (9.23)$$



(a) Bulk leakage currents

 

(b) Logic 1 voltage decay

Figure 9.15 Charge leakage problem

Outline

- ❑ Mirror Circuits
- ❑ Pseudo-nMOS
- ❑ Tri-State Circuits
- ❑ Clocked CMOS
- ❑ Dynamic CMOS Logic Circuits
- ❑ Dual-Rail Logic Networks

Dynamic CMOS Logic Circuits (1/2)

- ❑ A dynamic logic gate uses clocking and charge storage properties of MOSFETs to implement logic operations
 - » Provide a *synchronized* data flow
 - » Result is valid only for a short period of time
 - » Less transistors, and may be faster than static cascades
- ❑ Based on the circuit in Figure 9.17
 - » The clock ϕ drives a complementary pair of transistors M_n and M_p
 - » An nFET array between the output node and ground to perform the logic function
 - » When $\phi = 0$, it is called *precharge phase*
 - » When $\phi = 1$, it is called *evaluation phase*

 


Figure 9.17 Basic dynamic logic gate

Dynamic CMOS Logic Circuits (2/2)

- A dynamic NAND3 is shown in Figure 9.18

$$f = \overline{a \cdot b \cdot c} \quad (9.24)$$

- When $f = 1$, *charge leakage* reduces the voltages held on the output node

 


Figure 9.18 Dynamic logic gate example

Charge Sharing Problem

- The origin of the charge sharing problem is the parasitic node capacitance C_1 and C_2 between FETs

- » When clock $\phi \rightarrow 1$, and the capacitor voltage V_1 and V_2 are both 0 V at this time, the total charge is

$$Q = C_{out} V_{DD} \quad (9.25)$$

- » The worst-case charge sharing condition is when the inputs are at $(a, b, c) = (1, 1, 0)$

$$V_{out} = V_2 = V_1 = V_f \quad (9.26) \quad (\text{When the current flow ceases})$$

 


Figure 9.19 Charge sharing circuit

- » The principle of conservation of charge

$$\begin{aligned} \Rightarrow Q &= C_{out} V_f + C_1 V_f + C_2 V_f \\ &= (C_{out} + C_1 + C_2) V_f \end{aligned} \quad (9.27)$$

$$\left(\frac{C_{out}}{C_{out} + C_1 + C_2} \right) < 1 \quad (9.30)$$

$$\Rightarrow Q = (C_{out} + C_1 + C_2) V_f = C_{out} V_{DD} \quad (9.28)$$

$$V_f < V_{DD} \quad (9.31)$$

$$\Rightarrow V_f = \left(\frac{C_{out}}{C_{out} + C_1 + C_2} \right) V_{DD} \quad (9.29)$$

$$C_{out} \gg C_1 + C_2 \quad (9.32)$$

Domino Logic (1/2)

- ❑ Domino logic is a CMOS logic style obtained by adding a static inverter to the output of the basic dynamic gate circuit
 - » Non-inverting
 - » Cascade operation
 - » “Domino chain reaction” that must start at the first stage and then propagate stage by stage to the output

 


Figure 9.20 Domino logic stage

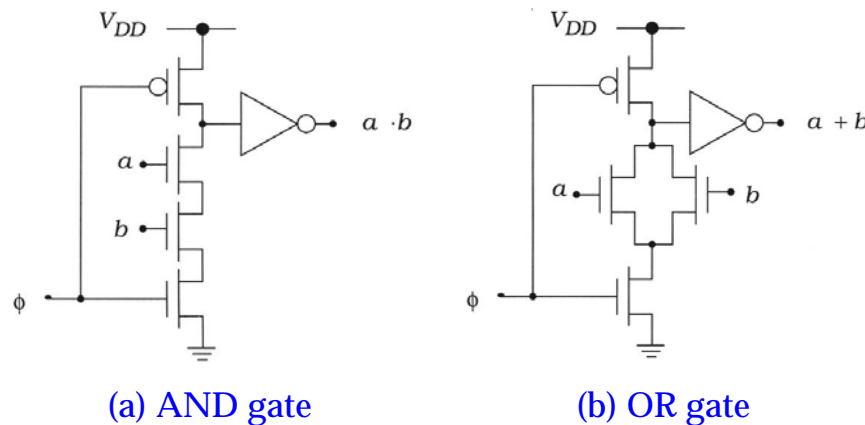


Figure 9.21 Non-inverting domino logic gates

 


Figure 9.22 Layout for domino AND gate

Domino Logic (2/2)

- Note that the operation indicates that domino gates are only useful in cascades

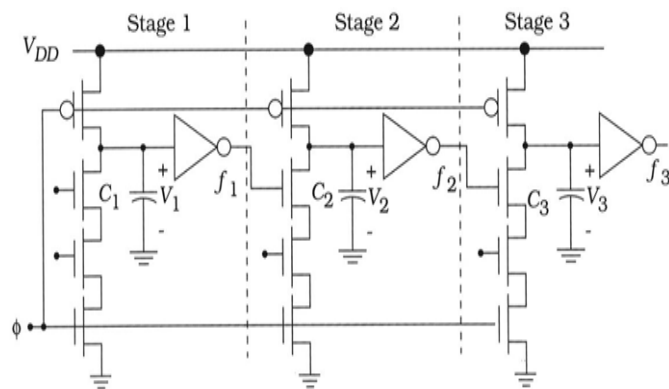


Figure 9.23 A domino cascade



 


Figure 9.24 Visualization of the domino effect

 


(a) Single-FET charge keeper

 

(b) Feedback controlled keeper

Figure 9.25 Charge-keeper circuits

 

$$\begin{aligned} f_1 &= G \\ f_2 &= F \cdot G \end{aligned} \quad (9.33)$$

Figure 9.26 Structure of a MODL circuit

Outline

- ❑ Mirror Circuits
- ❑ Pseudo-nMOS
- ❑ Tri-State Circuits
- ❑ Clocked CMOS
- ❑ Dynamic CMOS Logic Circuits
- ❑ Dual-Rail Logic Networks

Dual-Rail Logic Networks

- ❑ *Single-rail logic*: the value of a variable is either a 0 or a 1 only
- ❑ *Dual-rail logic*: both the variable x and its complement \bar{x} are used to form the difference

$$f_x = (x - \bar{x}) \quad (9.35)$$

$$\frac{df_x}{dt} = \left(\frac{dx}{dt} - \frac{d\bar{x}}{dt} \right) \quad (9.36)$$

$$\frac{d\bar{x}}{dt} \approx - \left| \frac{dx}{dt} \right| \quad (9.37)$$

$$\frac{df_x}{dt} \approx 2 \left| \frac{dx}{dt} \right| \quad (9.38)$$

Differential Cascode Voltage Switch Logic, DCVS (1/2)

- DCVS or differential CVSL (CVSL) provides for dual-rail logic gates, and the out results f and \bar{f} are held until the inputs induce a change



 


Figure 9.27 Structure of a CVSL logic gate

 

(a) AND/NAND

 

(b) OR/NOR

Figure 9.28 CVSL gate example

Complementary Pass-Transistor Logic


- Complementary Pass-Transistor (CPL): an dual-rail tech. that is based on nFET logic equations

$$f = a \cdot b + \bar{a} \cdot a \quad (9.41)$$

$$\Rightarrow a \cdot \bar{b} + \bar{a} = \bar{a} + \bar{b} = \overline{a \cdot b} \quad (9.42)$$

- CPL has several 2-input gates that can be created by using the same transistor topology with different input sequences

 
- » Less layout area
- » However, threshold will be loss and the fact that an input variable may have to drive more than one FET terminal



(a) AND gate

(b) AND/NAND array

Figure 9.32 CPL AND/NAND circuit

 

(a) OR/NOR

(b) XOR/XNOR

Figure 9.33 2-input CPL arrays